

 
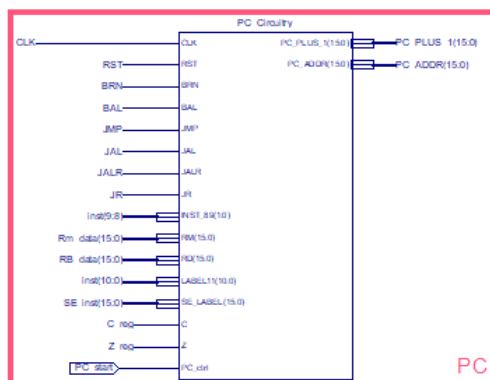
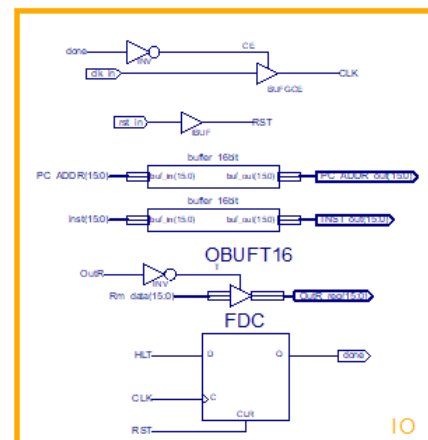
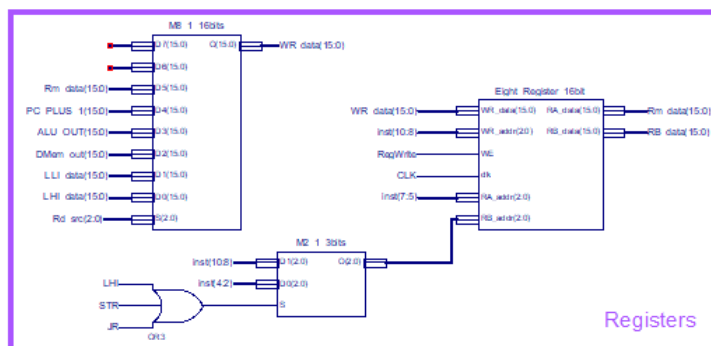


Schematic Entry


Datapath

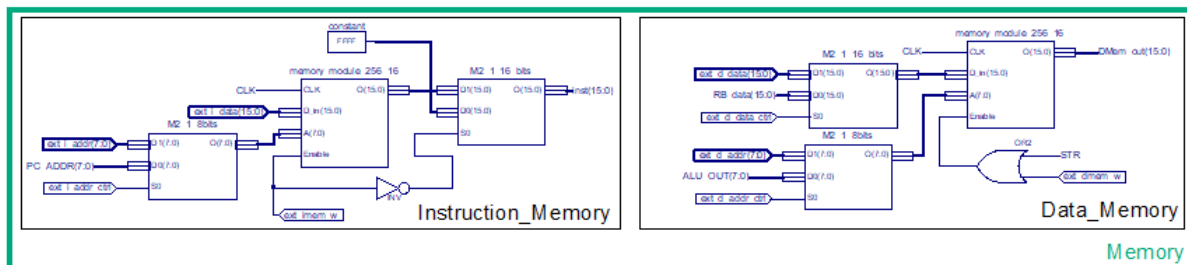

Datapath

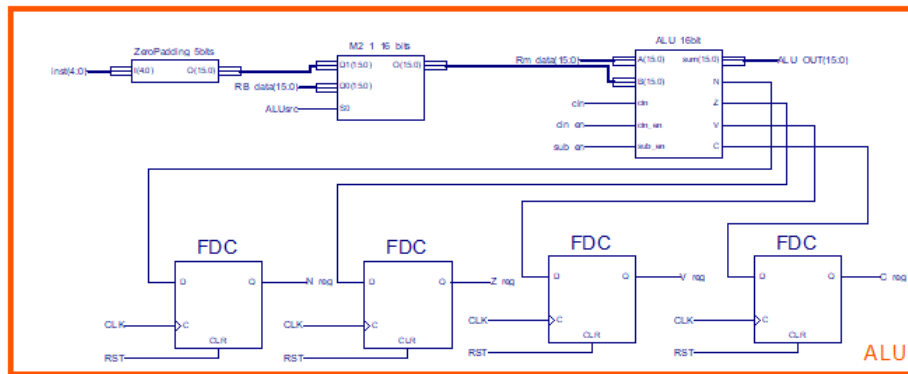


Controller

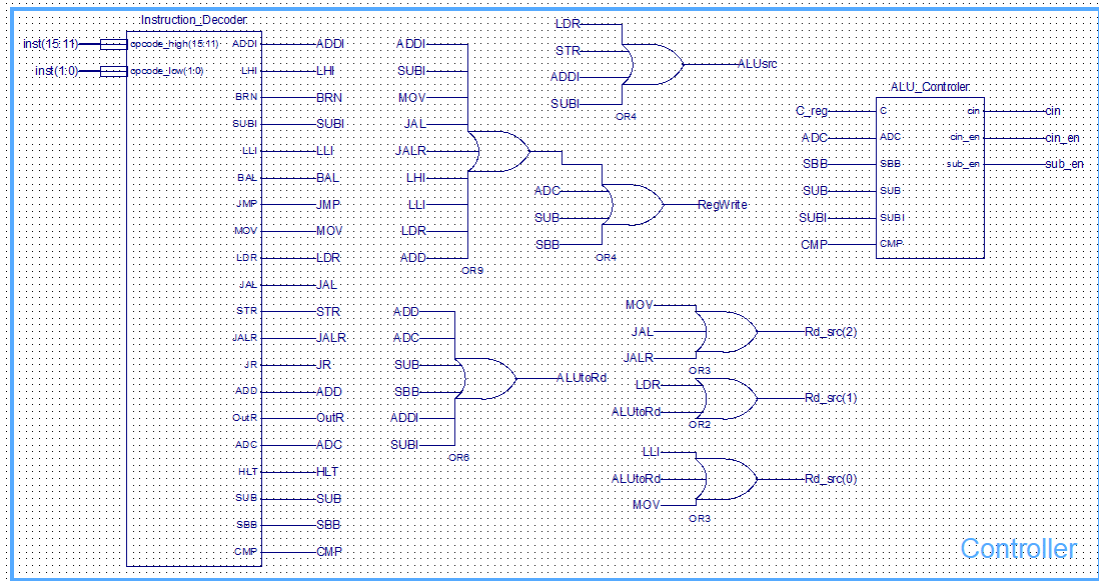

Controller




Registers

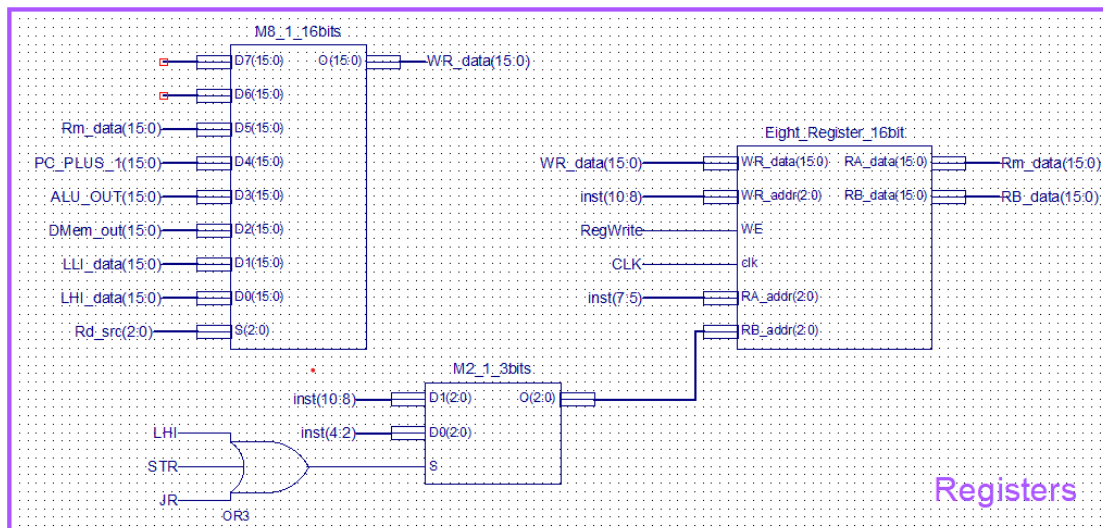


Registers


Eight_Register_16bit

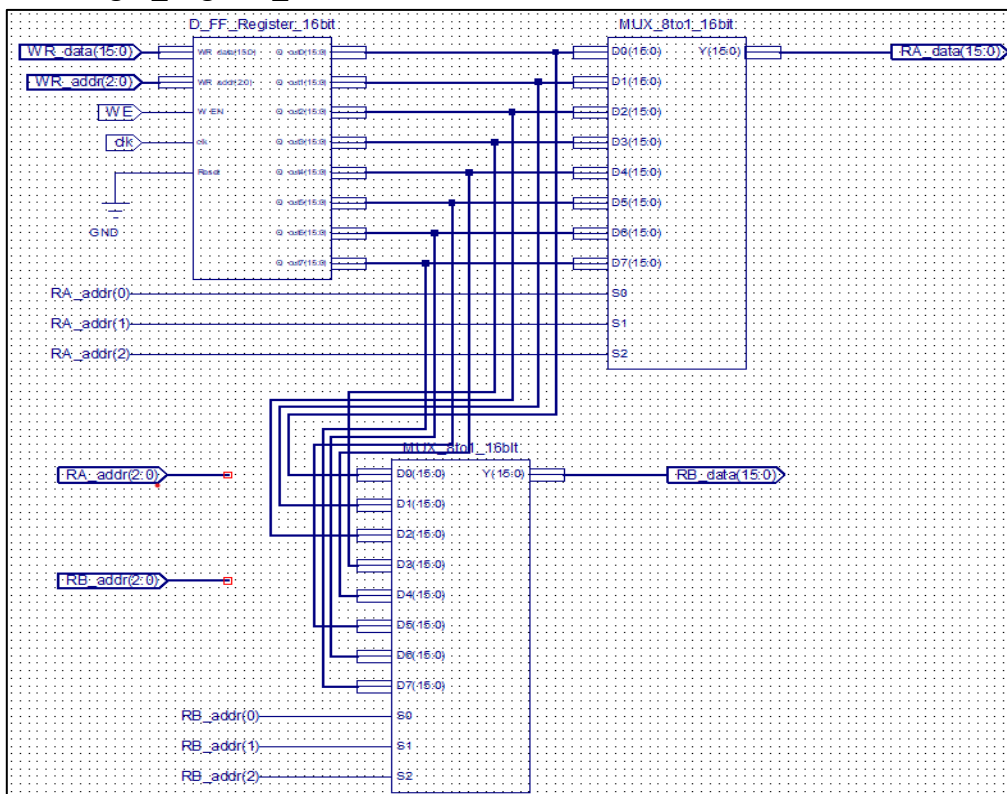


D_ff_Register_16bit

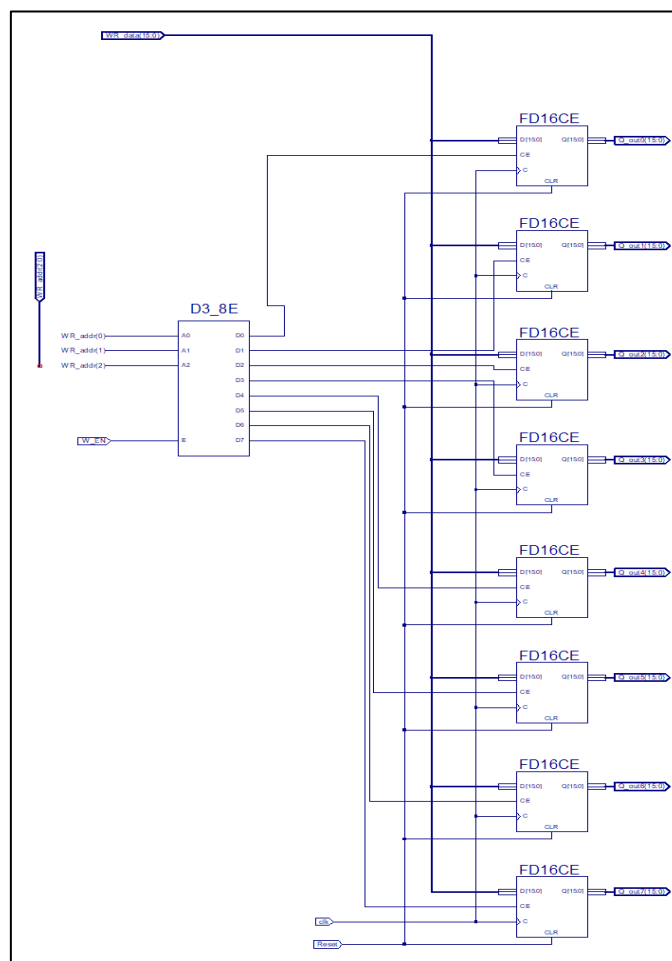


ALU

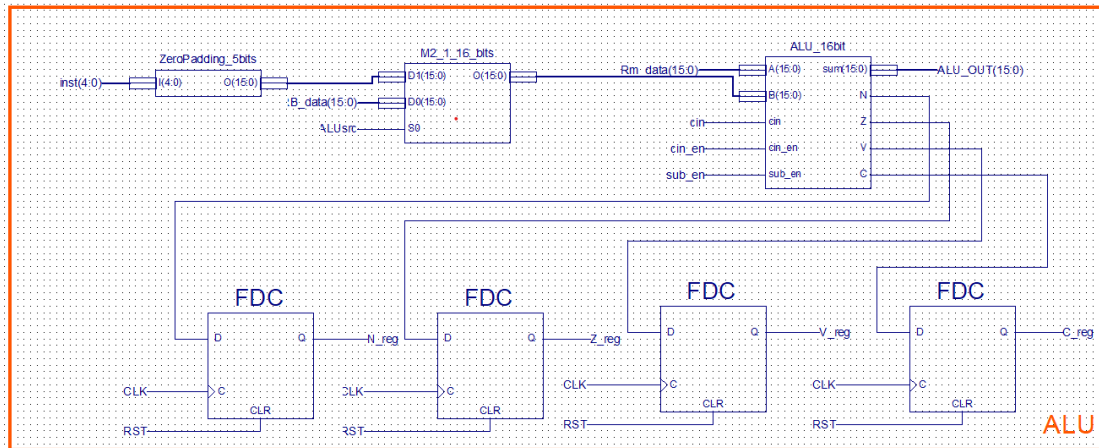


ALU_16bit

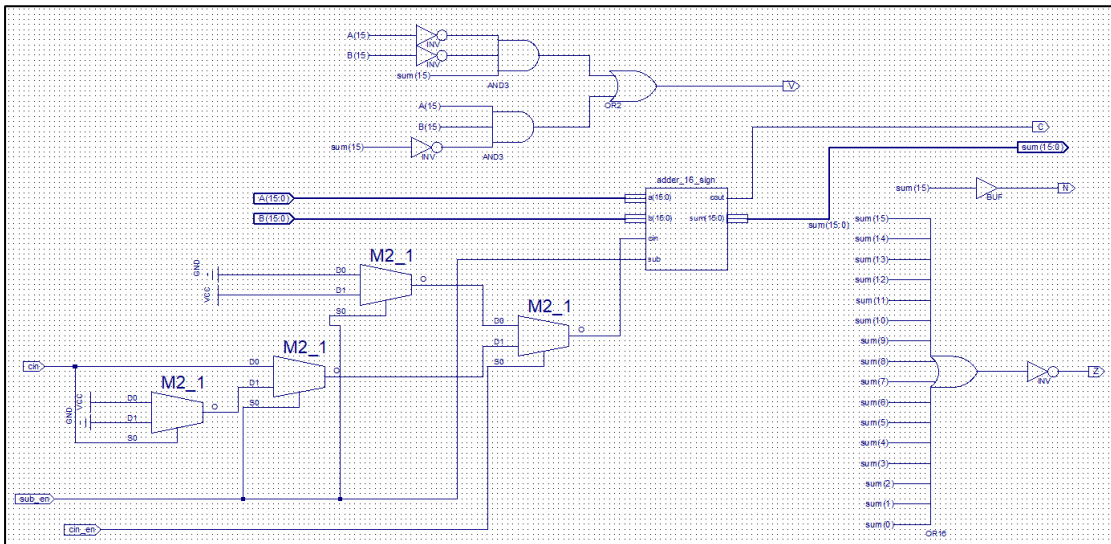


Adder_16_sign

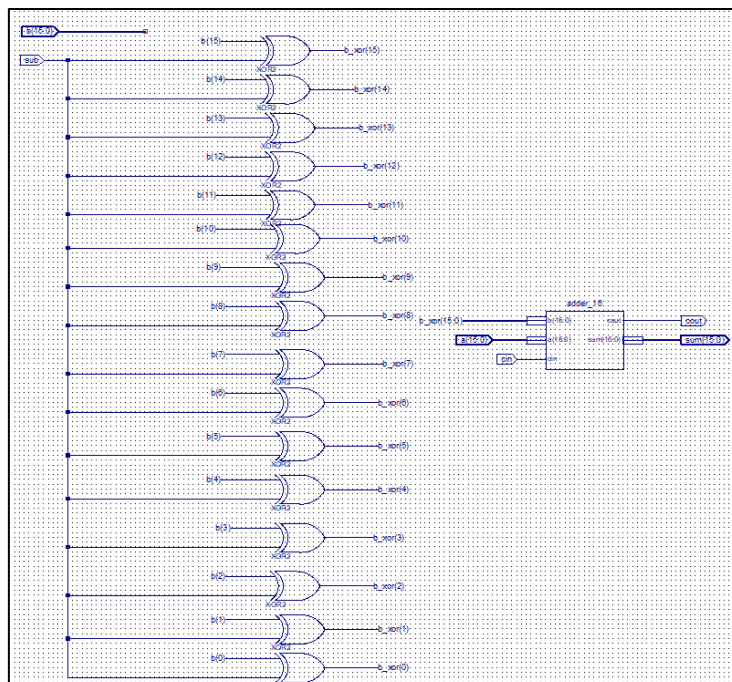


Adder_16

 


fulladder

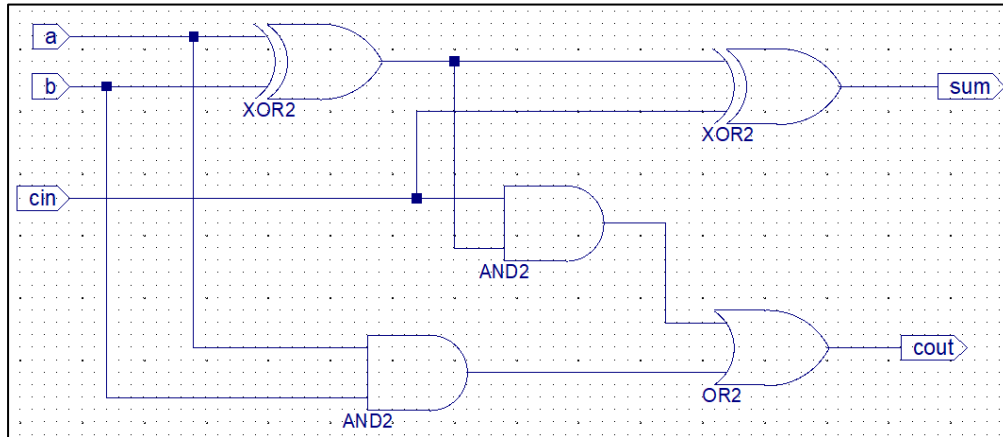


Memory

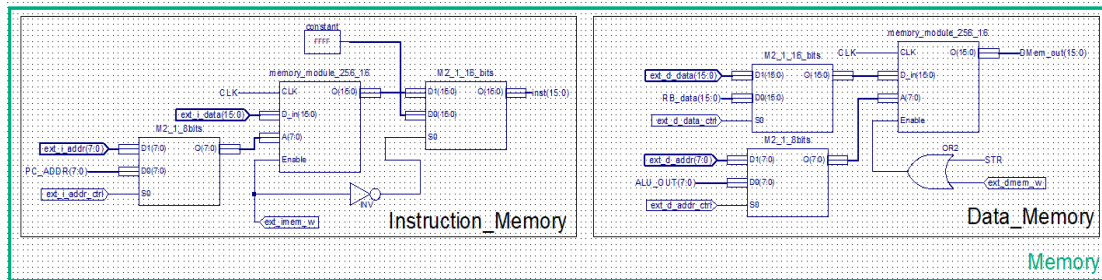


Instruction_Memory

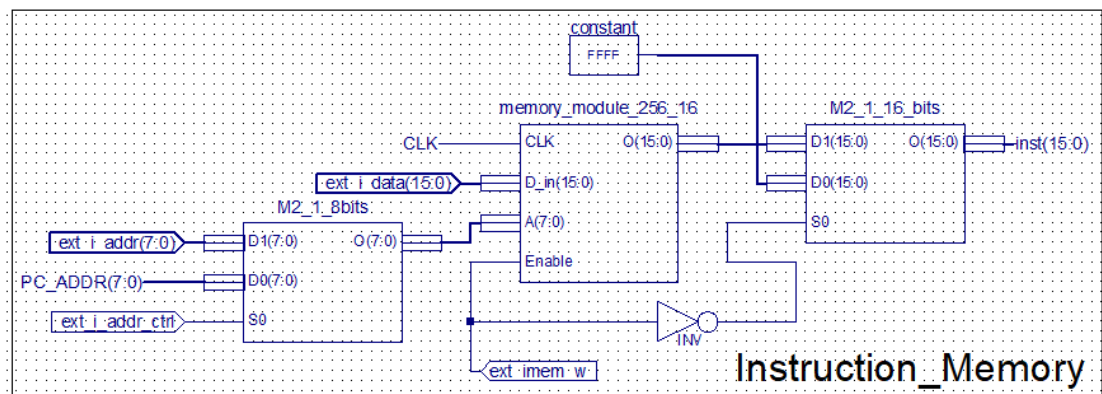


Data_Memory

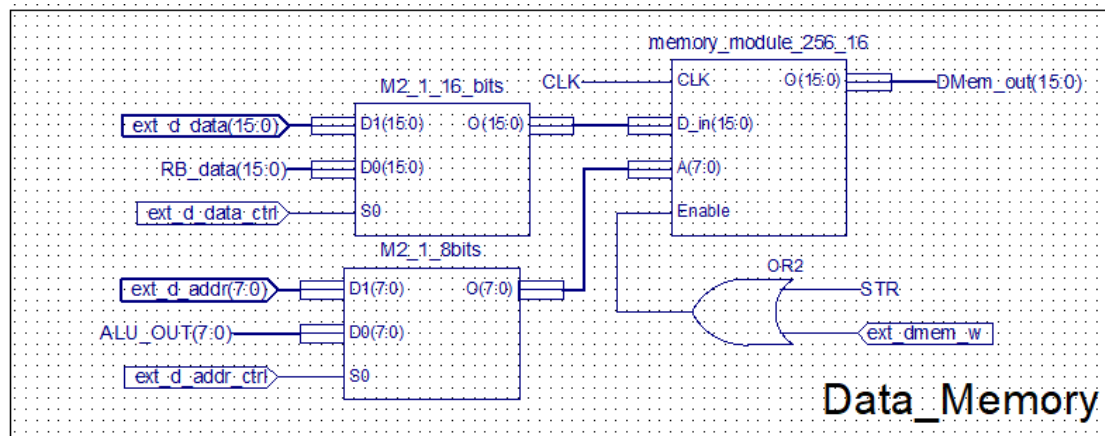


Memory_module_256_16

 

PC

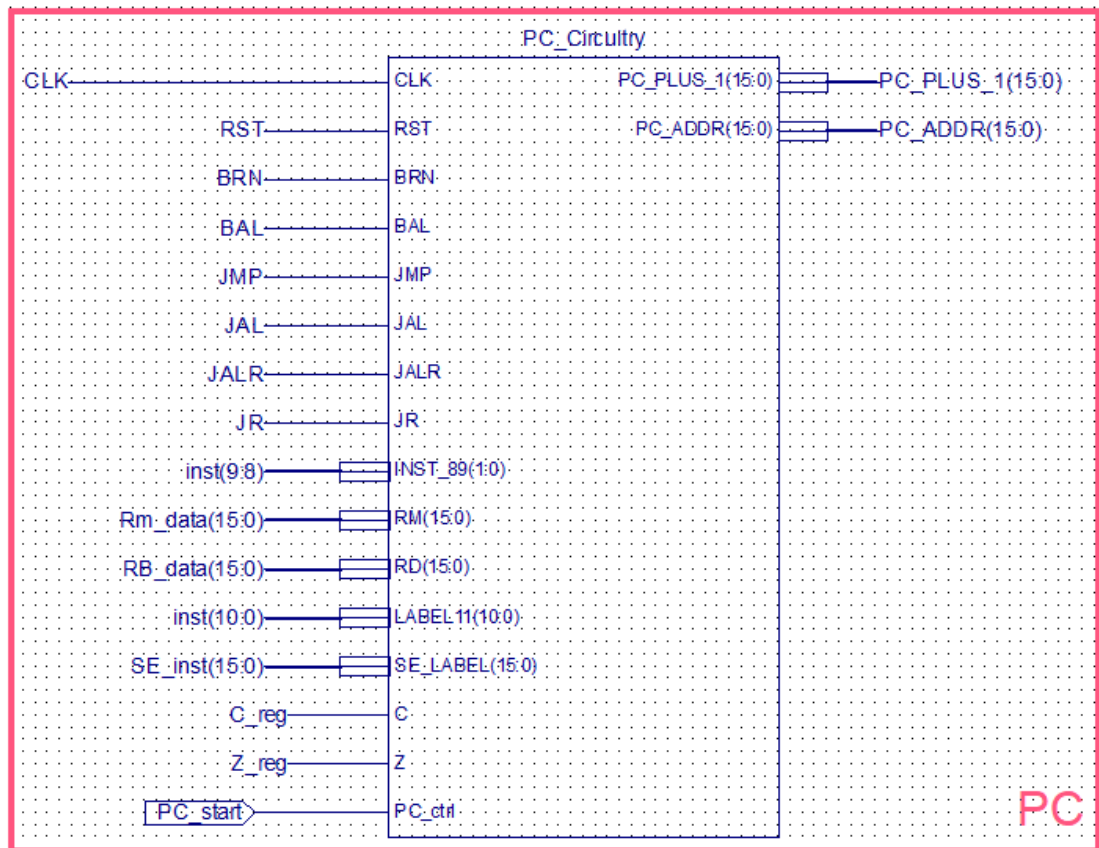


PC_Circuitry

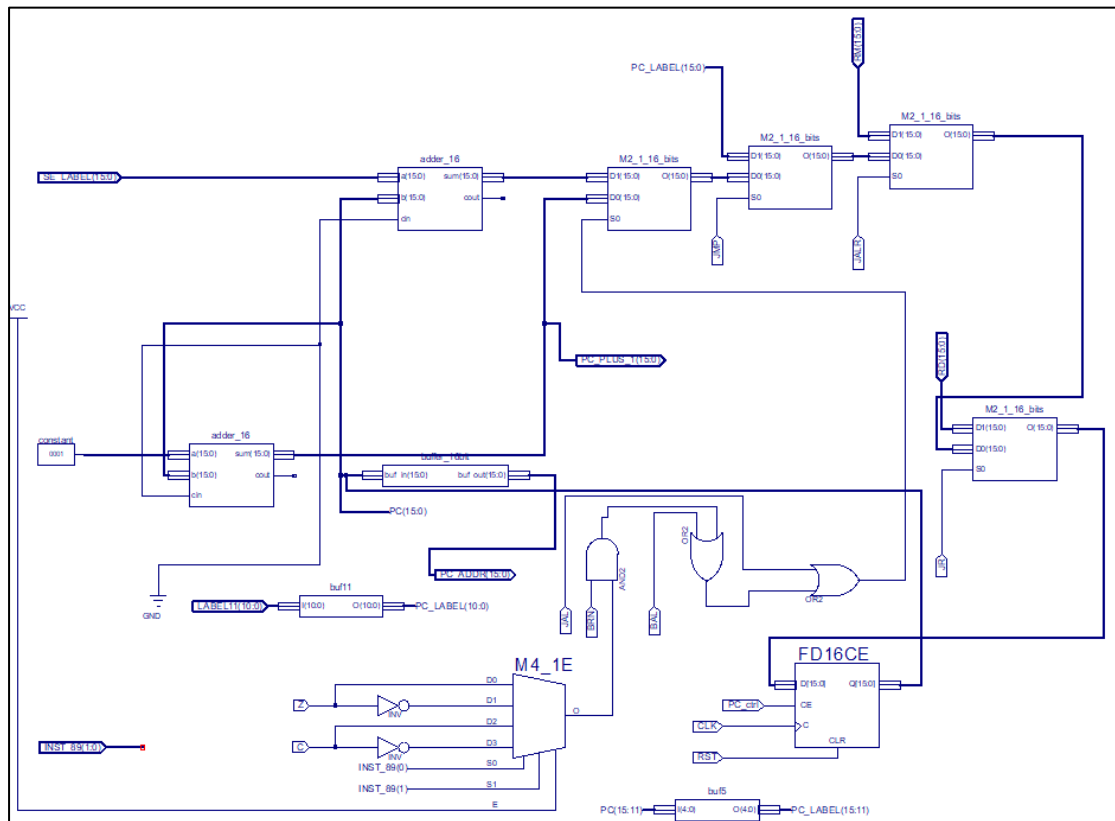




Controller

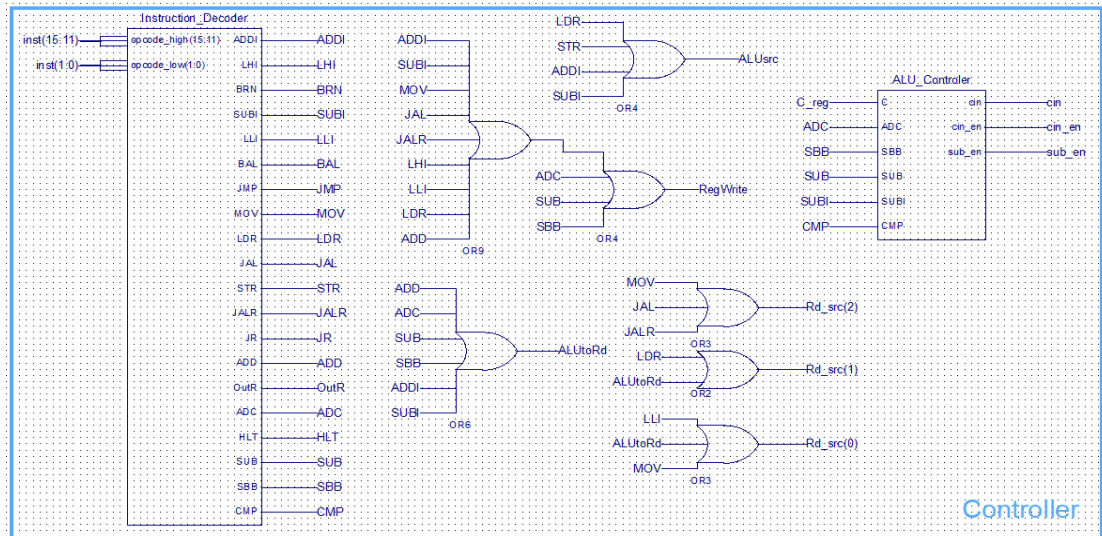


Controller




Instruction_Decoder

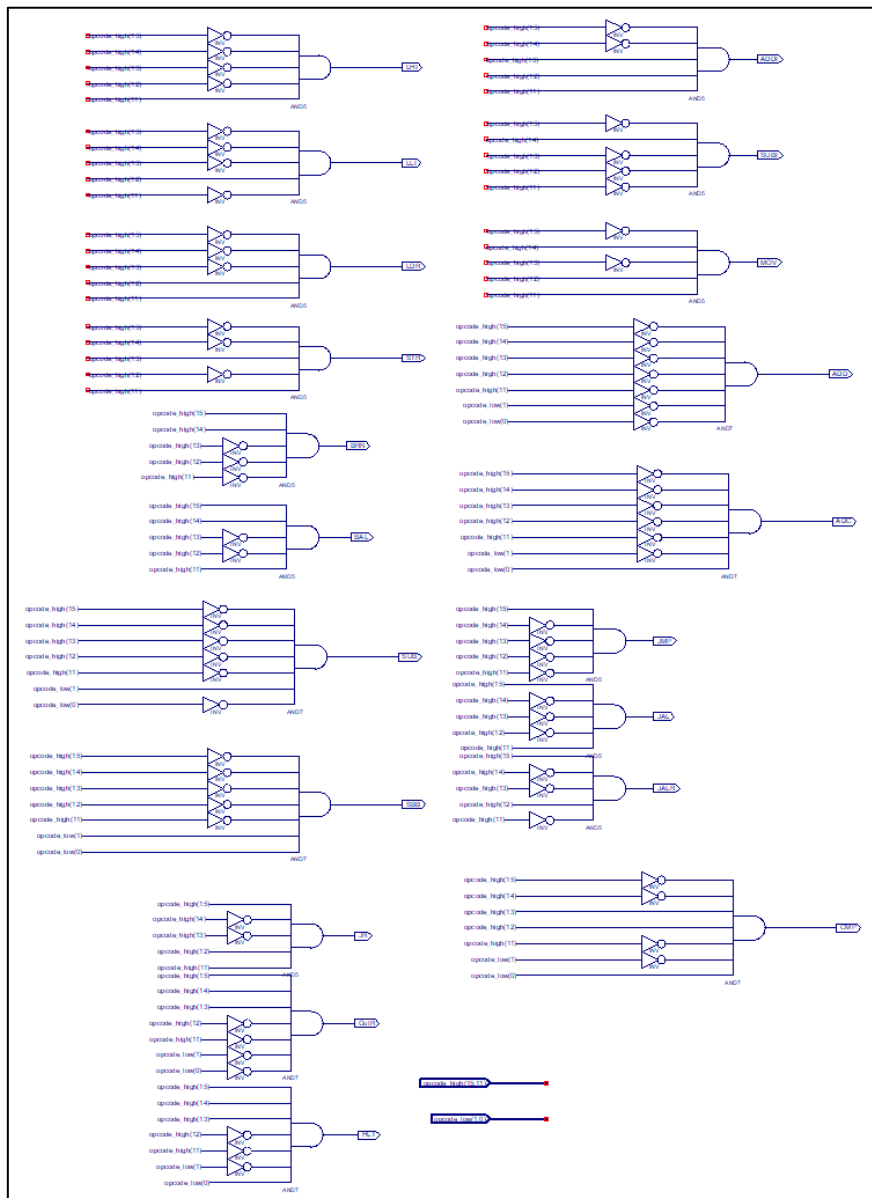


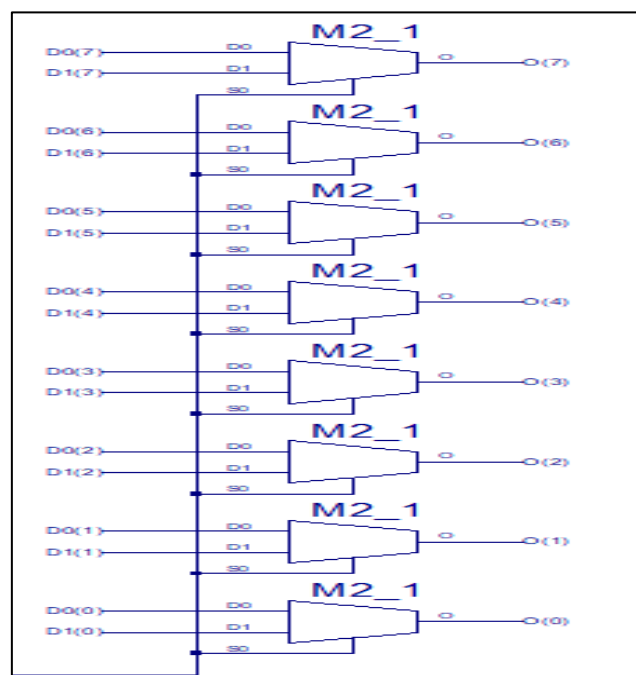


2 對 1 多工器(16bit)

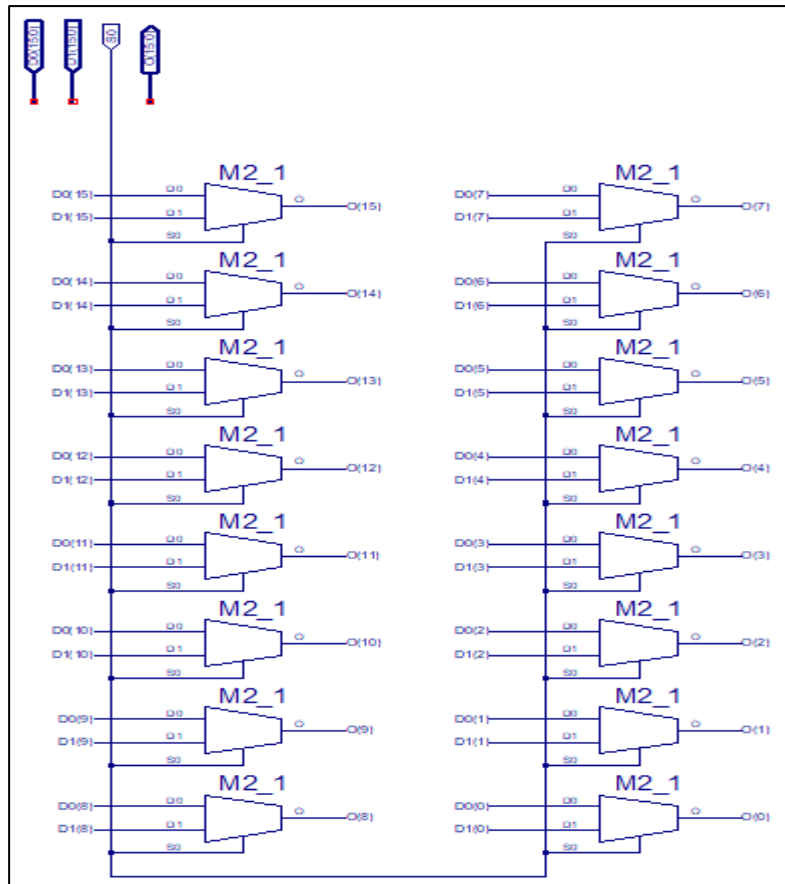


2 對 1 多工器(3bit)

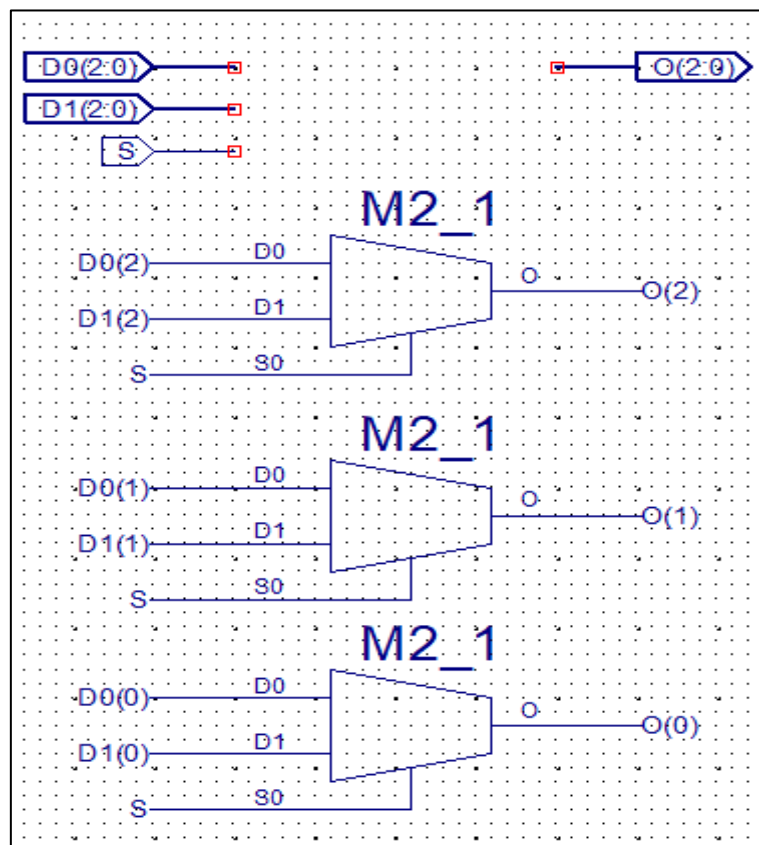


8 對 1 多工器(16bit)

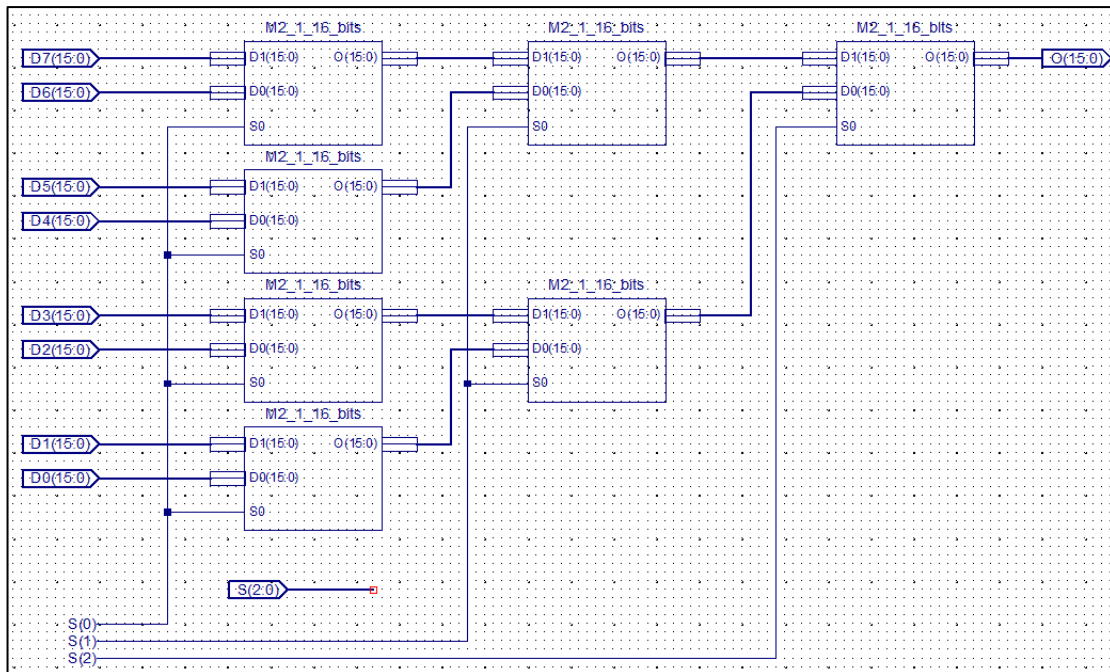


ImmediateGenerator(8to16)

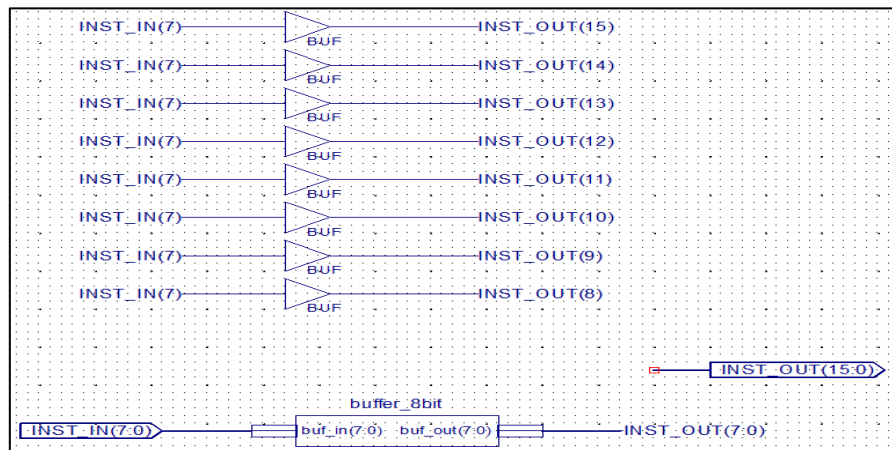


Zero extension

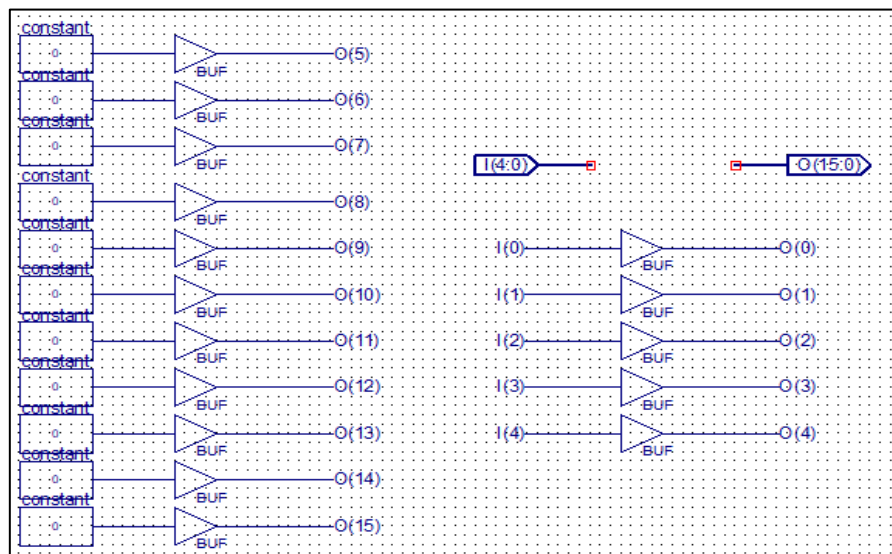

ImmediateGenerator(5to16)

 


4 對 1 多工器(16bit)

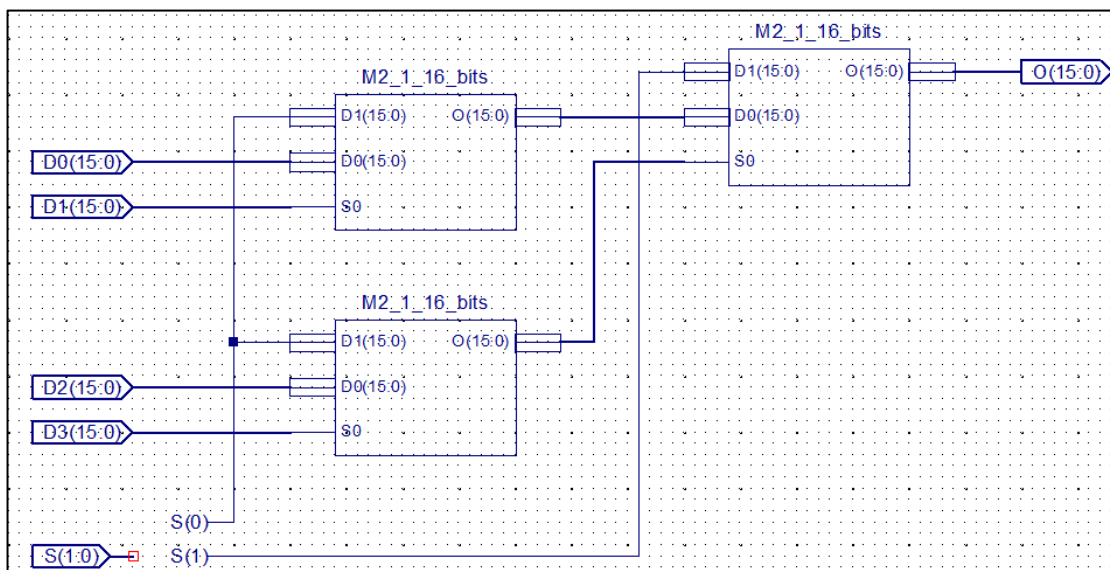
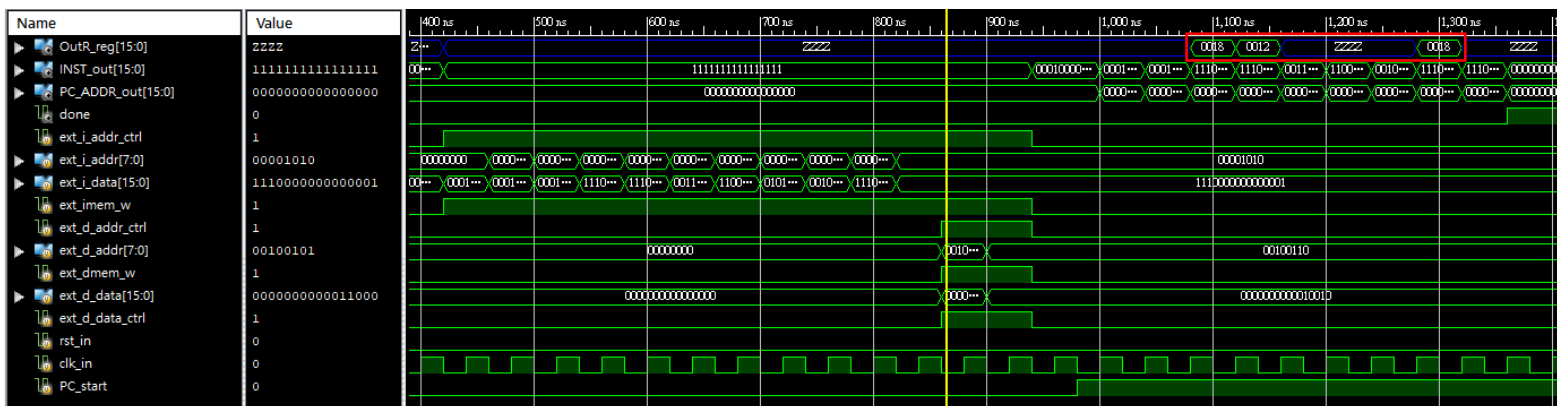
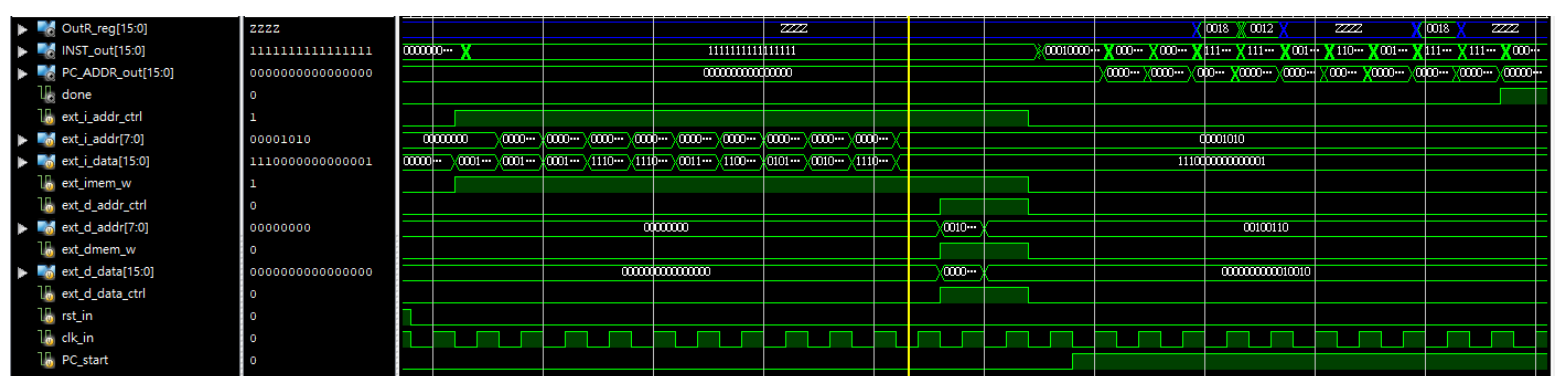


Verification

1. Find the minimum and maximum from two numbers in memory.

 Assembly code

```
Main:
00    LLI R0, #25
02    LDR R1, R0, #0
04    LDR R2, R0, #1
06    OUTR R1
08    OUTR R2
0A    CMP R1, R2
0C    BCS R1_bigger
0E    MOV R1, R2
R1_bigger:
10    STR R1, R0, #2
12    OUTR R1
14    HLT
```

 Behavioral Post-Route

可以觀察到一開始記憶體裡面的值為 12H 和 18H，而在指令執行完後會找到最大值 18H 並輸出。

2. Add two numbers in memory and store the result in another memory location.


Assembly code

```


Main:
00  LLI R0, #25
02  LDR R1, R0, #0
04  LDR R2, R0, #1
06  OUTR R1
08  OUTR R2
0A  ADD R3, R1, R2
0C  STR R3, R0, #2
0E  OUTR R3
10  HLT

```

Behavioral

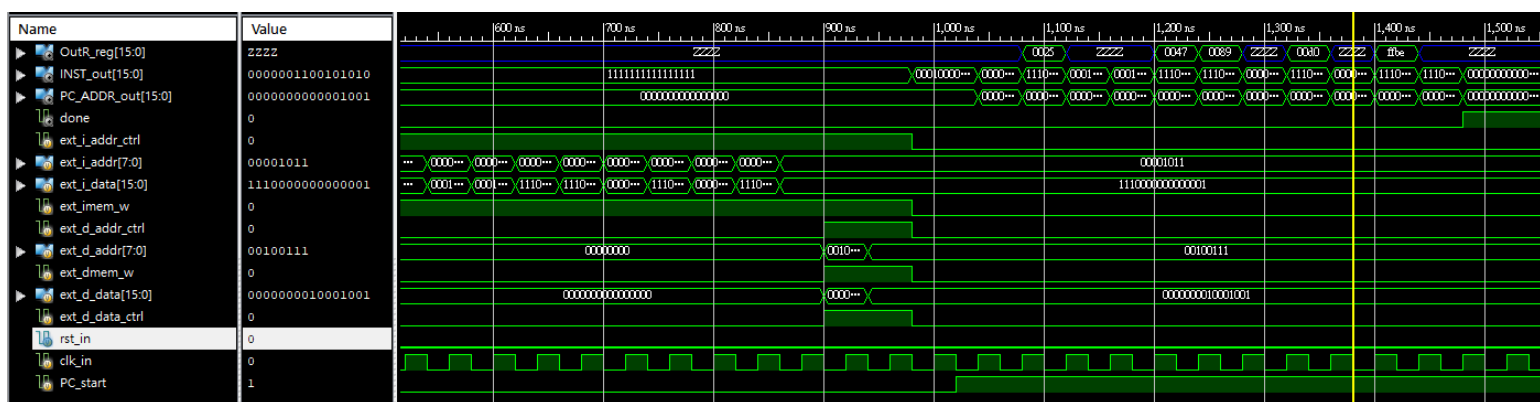

Post-Route

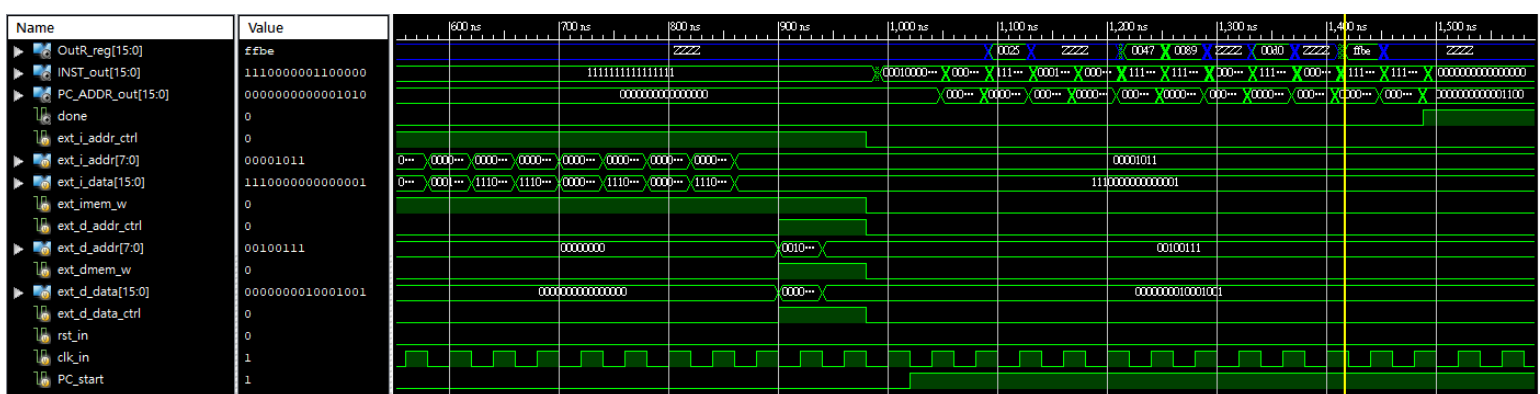

把 47H 存在記憶體位址 0025H，0089H 存在記憶體位址 0026H，將兩數相加得到結果 00D0H，相減得到結果 FFBEH。

3. Add ten numbers in consecutive memory locations.


Assembly code

```


Main:
00    LLI R0, #25
02    LLI R3, #10
04    LLI R4, #1
06    LLI R2, #0
Loop:
08    LDR R1, R0, #0
0A    OUTR R1
0C    ADD R2, R2, R1
0E    ADDI R0, R0, 1

10    SUBI R3, R3, 1
12    CMP R3, R4
14    BCS Loop
16    STR R2, R0, #5
18    OUTR R2
1A    HLT
  
```


Behavioral

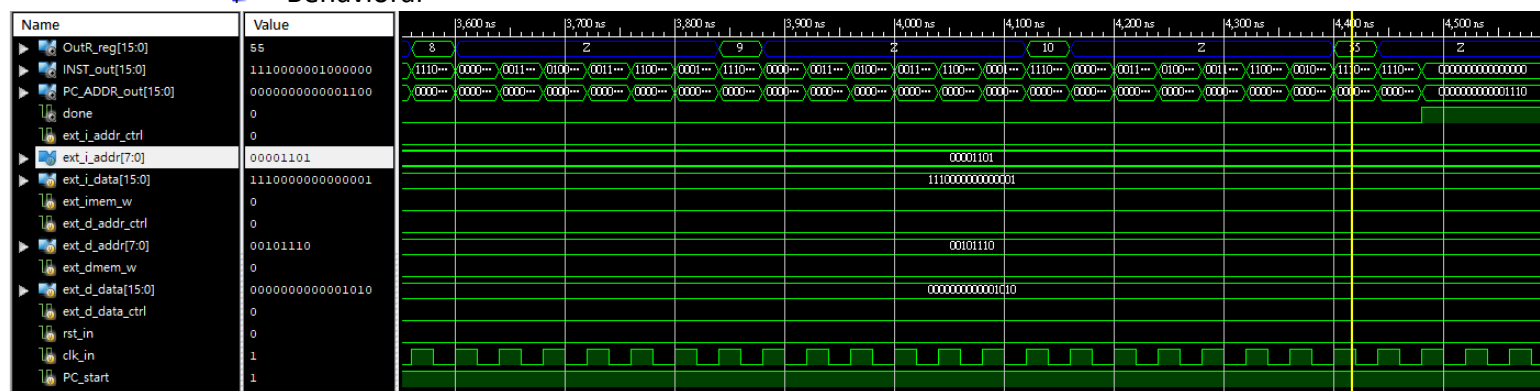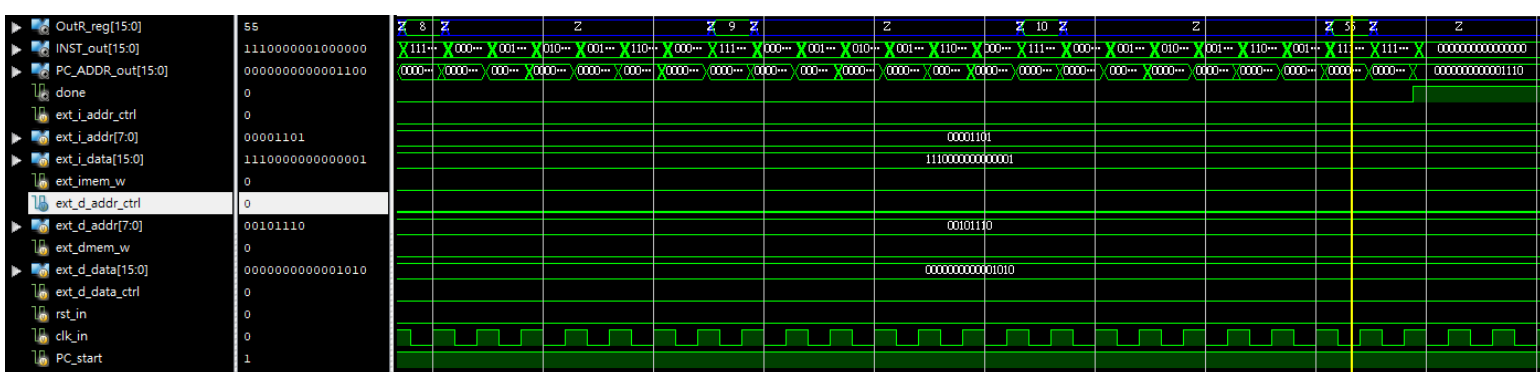
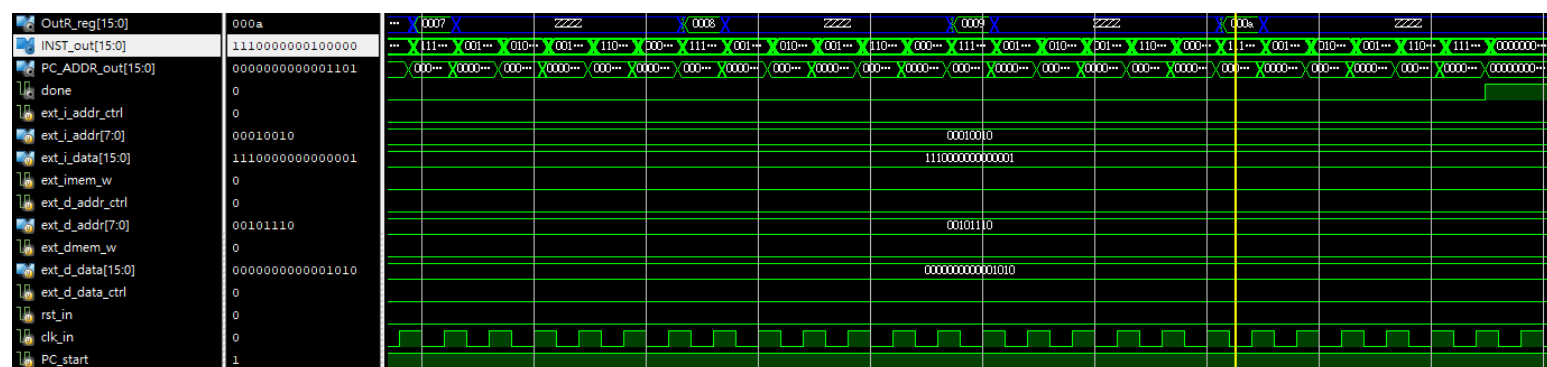


Post-Route



存在記憶體的值為1~10，可以看到結果會將每次運算的值輸出出來，也就是會計算 $(1+2+3+\dots+9+10)=55$ ，並且得到 55 的正確答案。

- 
- Assembly code


 Behavioral

可以看到最後的輸出是 8...9...10，因為我們是將 memory 裡面的 1~10，搬到另一個記憶體位址，我們再搬完後去查看記憶體的位址裡面是否為 1~10，可以發現 move 成功。


Hardware

Device Utilization Summary:				
Slice Logic Utilization:				
Number of Slice Registers:	147	out of	30,064	1%
Number used as Flip Flops:	147			
Number used as Latches:	0			
Number used as Latch-thrus:	0			
Number used as AND/OR logics:	0			
Number of Slice LUTs:	579	out of	15,032	3%
Number used as logic:	451	out of	15,032	3%
Number using O6 output only:	439			
Number using O5 output only:	0			
Number using O5 and O6:	12			
Number used as ROM:	0			
Number used as Memory:	128	out of	3,664	3%
Number used as Dual Port RAM:	0			
Number used as Single Port RAM:	128			
Number using O6 output only:	0			
Number using O5 output only:	0			
Number using O5 and O6:	128			
Number used as Shift Register:	0			
Slice Logic Distribution:				
Number of occupied Slices:	242	out of	3,758	6%
Number of MUXCYs used:	0	out of	7,516	0%
Number of LUT Flip Flop pairs used:	662			
Number with an unused Flip Flop:	515	out of	662	77%
Number with an unused LUT:	83	out of	662	12%
Number of fully used LUT-FF pairs:	64	out of	662	9%
Number of slice register sites lost to control set restrictions:	0	out of	30,064	0%
A LUT Flip Flop pair for this architecture represents one LUT paired with one Flip Flop within a slice. A control set is a unique combination of clock, reset, set, and enable signals for a registered element. The Slice Logic Distribution report is not meaningful if the design is over-mapped for a non-slice resource or if Placement fails.				
IO Utilization:				
Number of bonded IOBs:	105	out of	250	42%
Specific Feature Utilization:				
Number of RAMB16BWRs:	0	out of	52	0%
Number of RAMB8BWRs:	0	out of	104	0%
Number of BUFIO2/BUFIO2_2CLKs:	0	out of	32	0%
Number of BUFIO2FB/BUFIO2FB_2CLKs:	0	out of	32	0%
Number of BUFG/BUFGMUXs:	1	out of	16	6%
Number used as BUFGs:	0			
Number used as BUFGMUX:	1			
Number of DCM/DCM_CLKGENs:	0	out of	4	0%
Number of ILOGIC2/ISERDES2s:	0	out of	272	0%
Number of IODELAY2/IODRP2/IODRP2_MCBs:	0	out of	272	0%
Number of OLOGIC2/OSERDES2s:	0	out of	272	0%
Number of BSCANs:	0	out of	4	0%
Number of BUFHs:	0	out of	160	0%
Number of BUFPLLs:	0	out of	8	0%
Number of BUFPLL_MCBs:	0	out of	4	0%
Number of DSP48A1s:	0	out of	38	0%
Number of GTPA1_DUALs:	0	out of	1	0%
Number of ICAPs:	0	out of	1	0%
Number of MCBs:	0	out of	2	0%
Number of PCIE_A1s:	0	out of	1	0%
Number of PCILOGICSEs:	0	out of	2	0%
Number of PLL_ADVs:	0	out of	2	0%
Number of PMVs:	0	out of	1	0%
Number of STARTUPs:	0	out of	1	0%
Number of SUSPEND_SYNCs:	0	out of	1	0%

FPGA VIEW

 

RTL VIEW:

 

Discussion

雖然之前有修過計算機組織，但是在經過這次的作業後，對於整個 CPU 的架構又更加的了解，困難的部分就是以前在寫 Verilog 時，可以直接對硬體行為做描述，但是畫 Schematic 時電路卻需要全部手動拉，所以腦中必須思考，我想要做這樣的動作，那我需要哪些硬體，因此需要更多的設計時間去想怎麼實現。另外，因為這次實作的 ISA 是之前較不熟悉的，因此在設計時，有時候會不了解這個 ISA 為什麼需要這個指令，在網路搜尋後，細細研讀，就會發現有些指令設計的精妙，也就是為什麼要如此設計，會有一種原來也可以這樣做的感覺，學習到很多，未來在設計硬體電路時，也不會一昧的亂打 Verilog，心中也會浮現那塊理想的電路。