


 
 
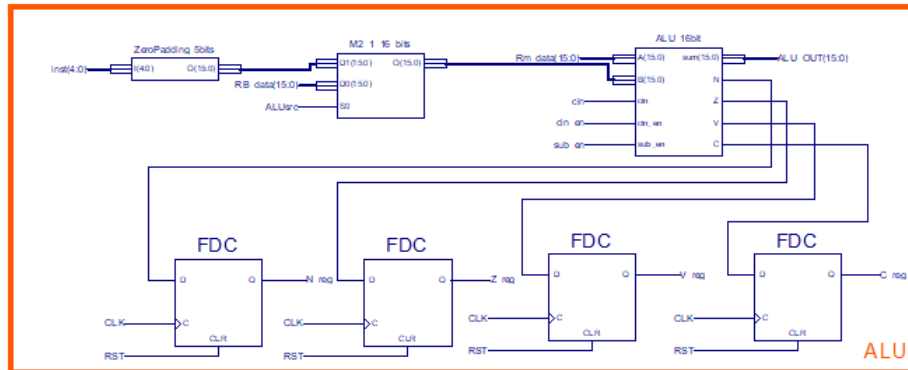
 


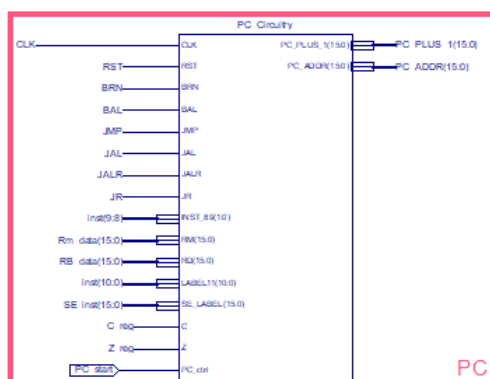

Datapath

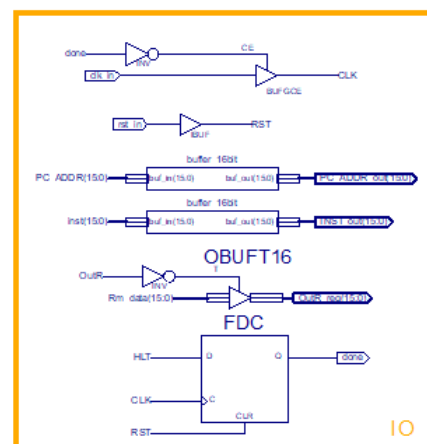


Memory

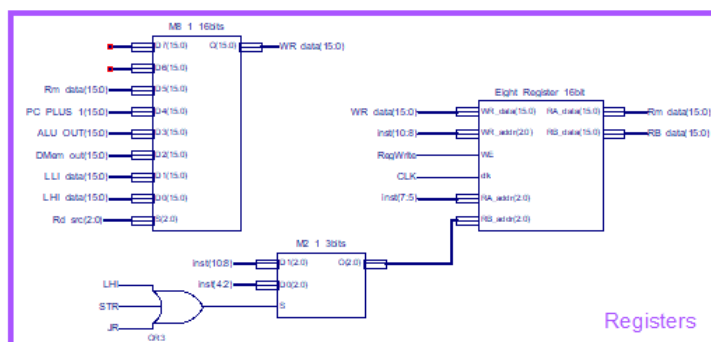

Datapath

Controller

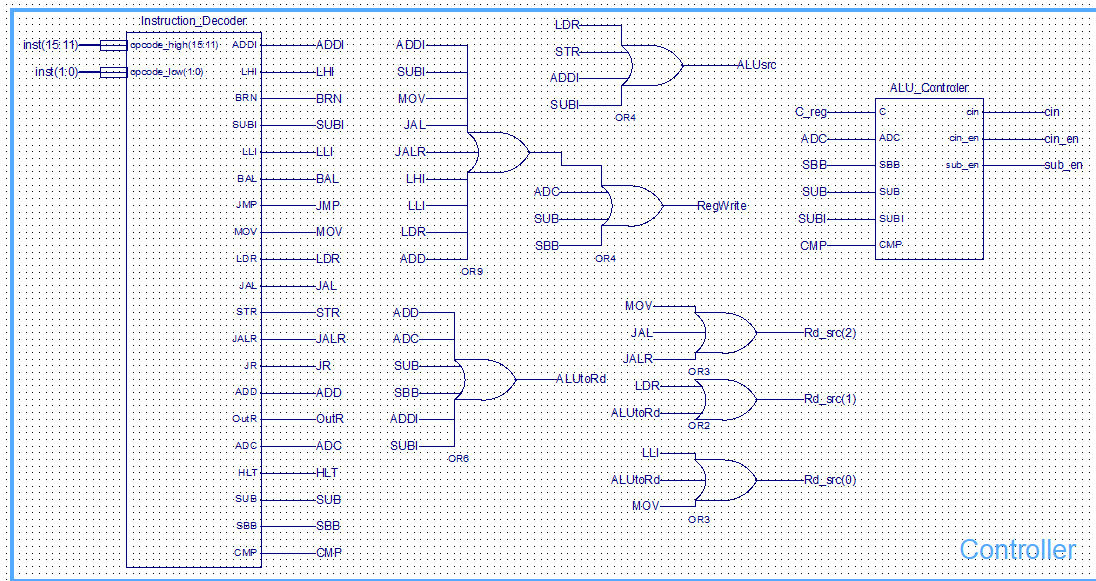

ALU

```

module ALU
(
    A,
    B,
    Cin,
    Sum,
    Sub,
    Cin_en,
    NZVC
);
    input [16-1:0] A;
    input [16-1:0] B;
    input Cin;
    input Cin_en;
    input Sub;
    output [16-1:0] Sum;
    output [4-1:0] NZVC;
    wire [16:0] result;
    wire Ci;
    assign Sum = result[15:0];
    assign NZVC[3] = result[15];
    assign NZVC[2] = ~(result[15:0]);
    assign NZVC[1] = (A[15] & B[15] & ~result[15]) (~A[15] & ~B[15] & result[15]);
    assign NZVC[0] = result[16];
    assign Ci = (Cin_en) ? Cin : 1'b0;
    assign result = (Sub) ? ((Cin_en) ? ({1'b0, A} + {1'b0, ~B} + 1'b1 + {16{~Ci}})
    : ({1'b0, A} + {1'b0, ~B} + 1'b1))
    : ((Cin_en) ? ({1'b0, A} + {1'b0, B} + {15{1'b0}}, Ci)
    : ({1'b0, A} + {1'b0, B}));
endmodule

```

Design:

ALU 的設計主要就是由幾個控制腳來決定要做甚麼工作，如果 Cin_en 為 1 則代表電路會有 Cin 輸入，如果 Sub 為 1 則代表 ALU 要做減法。NZVC 的 V

代表 overflow，而當 A,B 的 sign bit 為 0，運算結果的 sign bit 為 1 或是 A,B

的 sign bit 為 1，運算結果的 sign bit 為 0，也就是正 + 正 = 負, 負 + 負 = 正時，

代表 APU 溢位了。

ALU_Controller

```
module ALU_Controller
(
    opcode,
    ALU_op,
    Sub,
    Cin_en
);
    input  [4:0] opcode;
    input  [1:0] ALU_op;
    output reg    Sub;
    output wire   Cin_en;

    assign Cin_en = (opcode == 5'b00000) ? ALU_op[0] : 1'b0;
    always @(*)
    begin
        case(opcode)
            5'b00000:
            begin
                case(ALU_op[1:0])
                    2'b00: Sub = 1'b0;
                    2'b01: Sub = 1'b0;
                    2'b10: Sub = 1'b1;
                    2'b11: Sub = 1'b1;
                    default: Sub = 1'b0;
                endcase
            end
            5'b00110: Sub = 1'b1;
            5'b01000: Sub = 1'b1;
            default:   Sub = 1'b0;
        endcase
    end
endmodule
```

Design:

透過 opcode 來判斷什麼時候要做減法以及會有 Cin 等等控制訊號

Memory

```
module Memory
(
    clk,
    addr,
    idata,
    w_enable,
    odata
);
    input          clk;
    input  [ 8-1:0] addr;
    input  [16-1:0] idata;
    input          w_enable;
    output [16-1:0] odata;

    wire  [16-1:0] odata;
    reg    [15:0] memory[0:255];

    assign odata = memory[addr];
    always@(posedge clk) begin
        if(w_enable) memory[addr] ≤ idata;
    end
endmodule
```

Design:

設計 Memory 供 Data 和 instruction 使用，當 write enable 致能時才會將輸入資料寫入。

RegisterFile

```
module RegisterFile
(
    clk,
    rst_n,
    we,
    ra_addr,
    rb_addr,
    wr_addr,
    wr_data,
    ra_data,
    rb_data
);
    input          clk;
    input          rst_n;
    input          we;
    input [3-1:0] ra_addr;
    input [3-1:0] rb_addr;
    input [3-1:0] wr_addr;
    input [16-1:0] wr_data;
    output [16-1:0] ra_data;
    output [16-1:0] rb_data;
    reg signed [15:0] register [0:7];

    assign ra_data = register[ra_addr];
    assign rb_data = register[rb_addr];
    always @(posedge clk or negedge rst_n)
    begin
        if (~rst_n) // Initial
        begin
            register[0] ≤ 16'd0; register[1] ≤ 16'd0; register
            [2] ≤ 16'd0; register[3] ≤ 16'd0;
            register[4] ≤ 16'd0; register[5] ≤ 16'd0; register
            [6] ≤ 16'd0; register[7] ≤ 16'd0;
        end
        else
        begin
            if (we) // Write
                register[wr_addr] ≤ wr_data;
            end
        end
    end
endmodule
```

Design:

設計 8 個 general purpose register，並且有兩個 address，給定特定的 address，register 就會將值讀出來，而當寫入致能時才會寫入資料

Controller

```
module Controller
```

```
(
```

```
    inst,
```

```
    ALU_src,
```

```
    RegWrite,
```

```
    MemWrite,
```

```
    RD_src,
```

```
    Mem_src,
```

```
    PC_src,
```

```
    Jmp,
```

```
    Jalr,
```

```
    Jr,
```

```
    OutR,
```

```
    Hlt,
```

```
    NZVC
```

```
);
```

```
    localparam LHI  = 5'b000001;
```

```
    localparam LLI  = 5'b000010;
```

```
    localparam LDR  = 5'b000011;
```

```
    localparam STR  = 5'b000101;
```

```
    localparam ALU  = 5'b000000;
```

```
    localparam CMP  = 5'b000110;
```

```
    localparam ADDI = 5'b000111;
```

```
    localparam SUBI = 5'b001000;
```

```
    localparam MOV  = 5'b001011;
```

```
    localparam BRN  = 5'b011000;
```

```
    localparam BAL  = 5'b011001;
```

```
    localparam JMP  = 5'b010000;
```

```
    localparam JAL  = 5'b010001;
```

```
    localparam JALR = 5'b010010;
```

```
    localparam JR   = 5'b010011;
```

```
    localparam OUT  = 5'b011100;
```

```

input wire [16-1:0] inst;
input wire [ 3:0] NZVC;
output reg ALU_src;
output reg RegWrite;
output reg MemWrite;
output reg RD_src;
output reg [2:0] Mem_src;
output reg PC_src;
output reg Jmp;
output reg Jalr;
output reg Jr;
output reg OutR;
output reg Hlt;

always @(*)
begin
    case (inst[15:11]) // Acturally use 5 bits
        LHI :
        begin
            ALU_src  = 1'b0;
            RegWrite = 1'b1;
            MemWrite = 1'b0;
            RD_src   = 1'b1;
            Mem_src  = 3'b000;
            PC_src   = 1'b0;
            Jmp      = 1'b0;
            Jalr     = 1'b0;
            Jr       = 1'b0;
            OutR     = 1'b0;
            Hlt      = 1'b0;
        end
        LLI :
        begin
            ALU_src  = 1'b0;
            RegWrite = 1'b1;
            MemWrite = 1'b0;
            RD_src   = 1'b0;
            Mem_src  = 3'b001;
        end
    endcase
end

```

```

        PC_src    = 1'b0;
        Jmp       = 1'b0;
        Jalr      = 1'b0;
        Jr        = 1'b0;
        OutR      = 1'b0;
        Hlt       = 1'b0;
    end
LDR :
begin
    ALU_src    = 1'b1;
    RegWrite   = 1'b1;
    MemWrite   = 1'b0;
    RD_src     = 1'b0;
    Mem_src    = 3'b010;
    PC_src     = 1'b0;
    Jmp        = 1'b0;
    Jalr       = 1'b0;
    Jr         = 1'b0;
    OutR       = 1'b0;
    Hlt        = 1'b0;
end
STR :
begin
    ALU_src    = 1'b1;
    RegWrite   = 1'b0;
    MemWrite   = 1'b1;
    RD_src     = 1'b1;
    Mem_src    = 3'b000;
    PC_src     = 1'b0;
    Jmp        = 1'b0;
    Jalr       = 1'b0;
    Jr         = 1'b0;
    OutR       = 1'b0;
    Hlt        = 1'b0;
end
ALU :
begin
    ALU_src    = 1'b0;

```



```
    RegWrite = 1'b1;
    MemWrite = 1'b0;
    RD_src   = 1'b0;
    Mem_src  = 3'b011;
    PC_src   = 1'b0;
    Jmp      = 1'b0;
    Jalr     = 1'b0;
    Jr       = 1'b0;
    OutR     = 1'b0;
    Hlt      = 1'b0;
```

end

CMP :

begin

```
    ALU_src = 1'b0;
    RegWrite = 1'b0;
    MemWrite = 1'b0;
    RD_src   = 1'b0;
    Mem_src  = 3'b000;
    PC_src   = 1'b0;
    Jmp      = 1'b0;
    Jalr     = 1'b0;
    Jr       = 1'b0;
    OutR     = 1'b0;
    Hlt      = 1'b0;
```

end

ADDI:

begin

```
    ALU_src = 1'b1;
    RegWrite = 1'b1;
    MemWrite = 1'b0;
    RD_src   = 1'b0;
    Mem_src  = 3'b011;
    PC_src   = 1'b0;
    Jmp      = 1'b0;
    Jalr     = 1'b0;
    Jr       = 1'b0;
    OutR     = 1'b0;
    Hlt      = 1'b0;
```

```

end
SUBI:
begin
    ALU_src    = 1'b1;
    RegWrite   = 1'b1;
    MemWrite    = 1'b0;
    RD_src     = 1'b0;
    Mem_src    = 3'b011;
    PC_src     = 1'b0;
    Jmp        = 1'b0;
    Jalr       = 1'b0;
    Jr         = 1'b0;
    OutR       = 1'b0;
    Hlt        = 1'b0;
end
MOV :
begin
    ALU_src    = 1'b0;
    RegWrite   = 1'b1;
    MemWrite    = 1'b0;
    RD_src     = 1'b0;
    Mem_src    = 3'b100;
    PC_src     = 1'b0;
    Jmp        = 1'b0;
    Jalr       = 1'b0;
    Jr         = 1'b0;
    OutR       = 1'b0;
    Hlt        = 1'b0;
end
BRN :
begin
    ALU_src    = 1'b0;
    RegWrite   = 1'b0;
    MemWrite    = 1'b0;
    RD_src     = 1'b0;
    Mem_src    = 3'b000;
    Jmp        = 1'b0;
    Jalr       = 1'b0;

```

```

Jr          = 1'b0;
OutR        = 1'b0;
Hlt         = 1'b0;
case (inst[9:8])
    2'b00: PC_src = ( NZVC[2]) ? 1'b1 : 1'b0;
    2'b01: PC_src = (!NZVC[2]) ? 1'b1 : 1'b0;
    2'b10: PC_src = ( NZVC[0]) ? 1'b1 : 1'b0;
    2'b11: PC_src = (!NZVC[0]) ? 1'b1 : 1'b0;
    default:PC_src = 1'b0;
endcase
end
BAL :
begin
    ALU_src  = 1'b0;
    RegWrite = 1'b0;
    MemWrite = 1'b0;
    RD_src   = 1'b0;
    Mem_src  = 3'b000;
    PC_src   = 1'b1;
    Jmp      = 1'b0;
    Jalr     = 1'b0;
    Jr       = 1'b0;
    OutR     = 1'b0;
    Hlt      = 1'b0;
end
JMP :
begin
    ALU_src  = 1'b0;
    RegWrite = 1'b0;
    MemWrite = 1'b0;
    RD_src   = 1'b0;
    Mem_src  = 3'b000;
    PC_src   = 1'b0;
    Jmp      = 1'b1;
    Jalr     = 1'b0;
    Jr       = 1'b0;
    OutR     = 1'b0;
    Hlt      = 1'b0;

```

```

end
JAL :
begin
    ALU_src  = 1'b0;
    RegWrite = 1'b1;
    MemWrite = 1'b0;
    RD_src   = 1'b0;
    Mem_src  = 3'b101;
    PC_src   = 1'b1;
    Jmp      = 1'b0;
    Jalr     = 1'b0;
    Jr       = 1'b0;
    OutR     = 1'b0;
    Hlt      = 1'b0;

```

```

end
JALR:
begin
    ALU_src  = 1'b0;
    RegWrite = 1'b1;
    MemWrite = 1'b0;
    RD_src   = 1'b0;
    Mem_src  = 3'b101;
    PC_src   = 1'b0;
    Jmp      = 1'b0;
    Jalr     = 1'b1;
    Jr       = 1'b0;
    OutR     = 1'b0;
    Hlt      = 1'b0;

```

```

end
JR :
begin
    ALU_src  = 1'b0;
    RegWrite = 1'b0;
    MemWrite = 1'b0;
    RD_src   = 1'b1;
    Mem_src  = 3'b000;
    PC_src   = 1'b0;
    Jmp      = 1'b0;

```

```

        Jalr      = 1'b0;
        Jr        = 1'b1;
        OutR      = 1'b0;
        Hlt       = 1'b0;
    end
    OUT :
    begin
        ALU_src   = 1'b0;
        RegWrite  = 1'b0;
        MemWrite  = 1'b0;
        RD_src    = 1'b0;
        Mem_src   = 3'b000;
        PC_src    = 1'b0;
        Jump      = 1'b0;
        Jalr      = 1'b0;
        Jr        = 1'b0;
        OutR      = ~inst[0];
        Hlt       = inst[0];
    end
    default: // None
    begin
        ALU_src   = 1'b0;
        RegWrite  = 1'b0;
        MemWrite  = 1'b0;
        RD_src    = 1'b0;
        Mem_src   = 3'b000;
        PC_src    = 1'b0;
        Jump      = 1'b0;
        Jalr      = 1'b0;
        Jr        = 1'b0;
        OutR      = 1'b0;
        Hlt       = 1'b0;
    end
endcase
end
endmodule

```

Design:

透過解析 opcode 的方式來設定各個 controller signal 的訊號，設計方法

就是透過 ISA 上所對應的指令集來解碼，並寫成 switch case 的方式

Single_Cycle_CPU

```
module Single_Cycle_CPU
(
    clk_in,
    rst_n,
    Out_R,
    PC_start,
    done,
    ext_imem_w,
    ext_i_addr,
    ext_i_data,
    ext_i_addr_ctrl,
    ext_dmem_w,
    ext_d_addr_ctrl,
    ext_d_data_ctrl,
    ext_d_addr,
    ext_d_data
);
    input          clk_in;
    input          rst_n;
    output [16-1:0] Out_R;
    output         done;
    input          PC_start;
    input          ext_i_addr_ctrl;
    input          ext_imem_w;
    input  [8-1:0] ext_i_addr;
    input  [16-1:0] ext_i_data;
    input          ext_d_data_ctrl;
    input          ext_dmem_w;
    input          ext_d_addr_ctrl;
    input  [8-1:0] ext_d_addr;
```

```

input  [16-1:0] ext_d_data;
wire      clk;
wire [16-1:0] PC_next;
reg  [16-1:0] PC;
wire [16-1:0] PC_plus;
wire [16-1:0] PC_plus_label;
wire [16-1:0] PC_branch;
wire [16-1:0] PC_jump;
wire [16-1:0] PC_jalr;
wire [16-1:0] inst;
wire [16-1:0] idata;
wire [ 8-1:0] iaddr;
wire ALU_src;
wire RegWrite;
wire MemWrite;
wire RD_src;
wire [2:0] Mem_src;
wire PC_src;
wire Jmp;
wire Jalr;
wire Jr;
wire OutR;
wire [ 3-1:0] rm_addr;
wire [ 3-1:0] rn_addr;
wire [ 3-1:0] rd_addr;
wire [16-1:0] rm_data;
wire [16-1:0] rn_data;
wire [16-1:0] rd_data;
wire [ 3-1:0] rb_addr;
wire [16-1:0] B;
wire [16-1:0] ALU_result;
wire [ 4-1:0] NZVC;
wire      Sub;
wire [16-1:0] data;
wire [16-1:0] ddata;
wire [ 8-1:0] daddr;
wire      dwe;
reg  [ 4-1:0] NZVC_reg;

```

```

assign clk = (done) ? 1'b0 : clk_in;
assign Out_R = (OutR) ? rm_data : {16{1'bz}} ;
always @(posedge clk or negedge rst_n) begin
    if(~rst_n||~PC_start) PC <= 16'd0; // Next PC value
    else PC <= PC_next; // Present PC value
end
assign rd_addr = inst[10:8];
assign rm_addr = inst[7:5];
assign rn_addr = inst[4:2];
assign dwe = MemWrite|ext_dmem_w;
assign PC_plus = PC + 1'b1;
assign PC_plus_label = PC + {{8{inst[7]}}, inst[7:0]};
always@(posedge clk) NZVC_reg <= NZVC;
MUX_2to1
#(
    .DATA_WIDTH (8 )
)
u_Instruction_Memory_MUX_2to1(
    .s (ext_i_addr_ctrl ),
    .i0 (PC[7:0] ),
    .i1 (ext_i_addr ),
    .o (iaddr )
);
MUX_2to1
#(
    .DATA_WIDTH (16 )
)
u_Instruction_Latch_MUX_2to1(
    .s (ext_imem_w ),
    .i0 ( idata ),
    .i1 (16'd1 ),
    .o (inst )
);
Memory u_Instruction_Memory(
    .clk (clk ),
    .addr (iaddr ),
    .idata (ext_i_data ),
    .wr (ext_imem_w ),

```



```

        .odata (idata      )
    );
MUX_2to1
#(
    .DATA_WIDTH (8 )
)
u_Data_Memory_ADDR_MUX_2to1(
    .s (ext_d_addr_ctrl ),
    .i0 (ALU_result[7:0] ),
    .i1 (ext_d_addr ),
    .o (daddr )
);
MUX_2to1
#(
    .DATA_WIDTH (16)
)
u_Data_Memory_Data_MUX_2to1(
    .s (ext_d_data_ctrl ),
    .i0 (rn_data ),
    .i1 (ext_d_data ),
    .o (ddata )
);
Memory u_Data_Memory(
    .clk (clk          ),
    .addr (daddr       ),
    .idata (ddata      ),
    .wr (dwe           ),
    .odata (data       )
);
Controller u_Controller(
    .inst (inst        ),
    .NZVC (NZVC_reg   ),
    .ALU_src (ALU_src  ),
    .RegWrite (RegWrite ),
    .MemWrite (MemWrite ),
    .RD_src (RD_src   ),
    .Mem_src (Mem_src  ),
    .PC_src (PC_src   ),

```

```

        .Jmp      (Jmp      ),
        .Jalr     (Jalr     ),
        .Jr       (Jr       ),
        .OutR     (OutR     ),
        .Hlt      (done )
    );

    RegisterFile u_RegisterFile(
        .clk      (clk      ),
        .rst_n    (rst_n    ),
        .we       (RegWrite ),
        .ra_addr  (rm_addr  ),
        .rb_addr  (rb_addr  ),
        .wr_addr  (rd_addr  ),
        .wr_data  (rd_data  ),
        .ra_data  (rm_data  ),
        .rb_data  (rn_data  )
    );

    MUX_2to1
    #(
        .DATA_WIDTH(3)
    )
    u_RB_MUX_2to1
    (
        .s  (RD_src  ),
        .i0 (rn_addr ),
        .i1 (rd_addr ),
        .o  (rb_addr )
    );

    MUX_2to1 u_ALU_MUX_2to1(
        .s  (ALU_src      ),
        .i0 (rn_data      ),
        .i1 ({11'd0,inst[4:0]}),
        .o  (B            )
    );

    ALU u_ALU(
        .A      (rm_data      ),
        .B      (B            ),

```

```

        .Cin    (NZVC_reg[0] ),
        .Sub    (Sub          ),
        .Cin_en (Cin_en       ),
        .Sum    (ALU_result   ),
        .NZVC   (NZVC         )
    );

    ALU_Conrtoller u_ALU_Conrtoller(
        .opcode (inst[15:11] ),
        .ALU_op (inst[1:0]   ),
        .Sub    (Sub          ),
        .Cin_en (Cin_en       )
    );

    MUX_8to1 u_MUX_8to1(
        .s (Mem_src           ),
        .i0 ({inst[7:0], rn_data[7:0]} ),
        .i1 ({8{1'b0}} , inst[7:0]} ),
        .i2 (data              ),
        .i3 (ALU_result        ),
        .i4 (rm_data           ),
        .i5 (PC_plus           ),
        .i6 ({16{1'b0}}        )
        .i7 ({16{1'b0}}        )
        .o (rd_data            )
    );


    MUX_2to1 u_PC_0_MUX_2to1(
        .s (PC_src            ),
        .i0 (PC_plus          ),
        .i1 (PC_plus_label    ),
        .o (PC_branch         )
    );

    MUX_2to1 u_PC_1_MUX_2to1(
        .s (Jmp                ),
        .i0 (PC_branch         ),
        .i1 ({PC[15:11], inst[10:0]} ),
        .o (PC_jump            )
    );


    MUX_2to1 u_PC_2_MUX_2to1(
        .s (Jalr                ),

```



✚ Eight_Register_16bit

 


✚ D_ff_Register_16bit

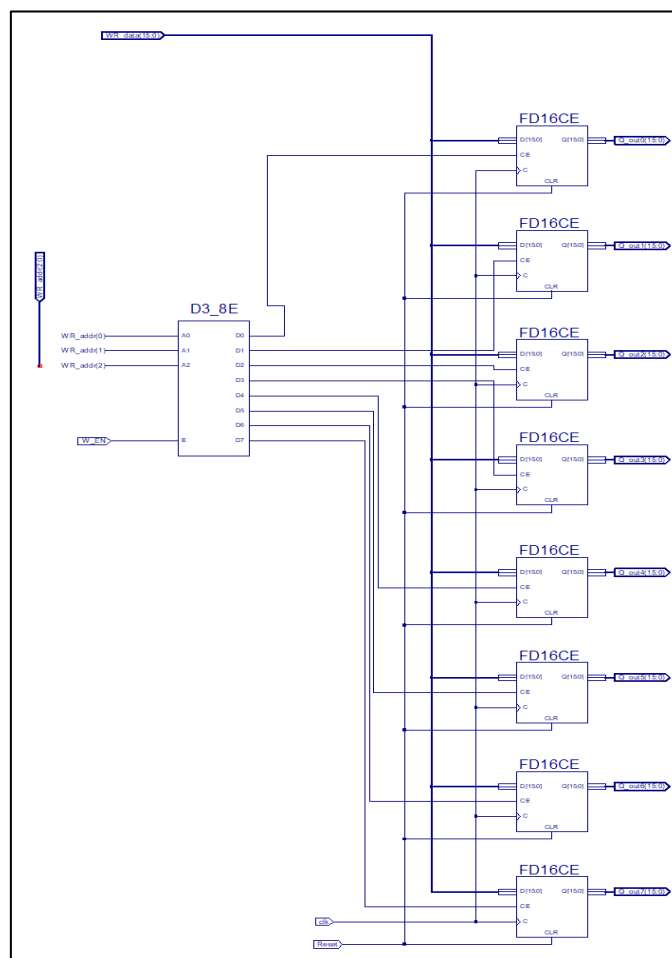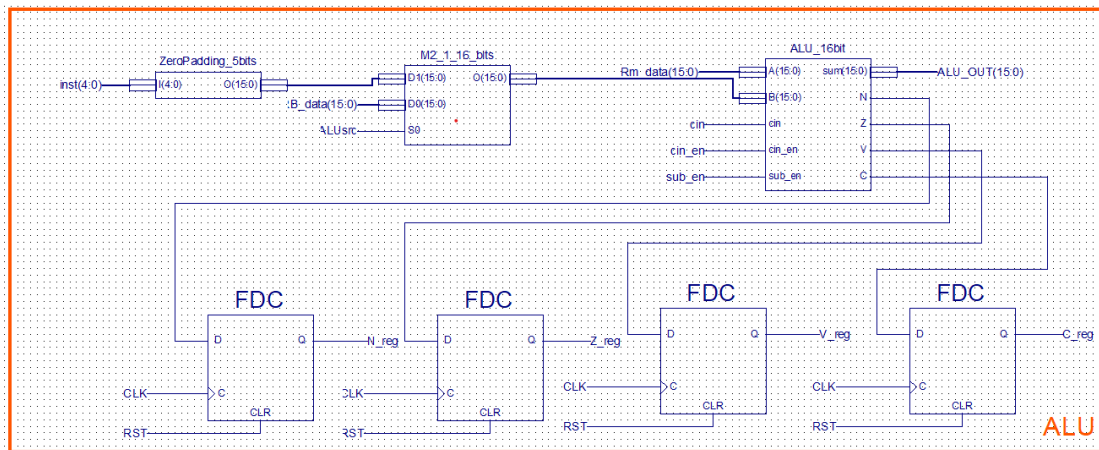


ALU




ALU_16bit

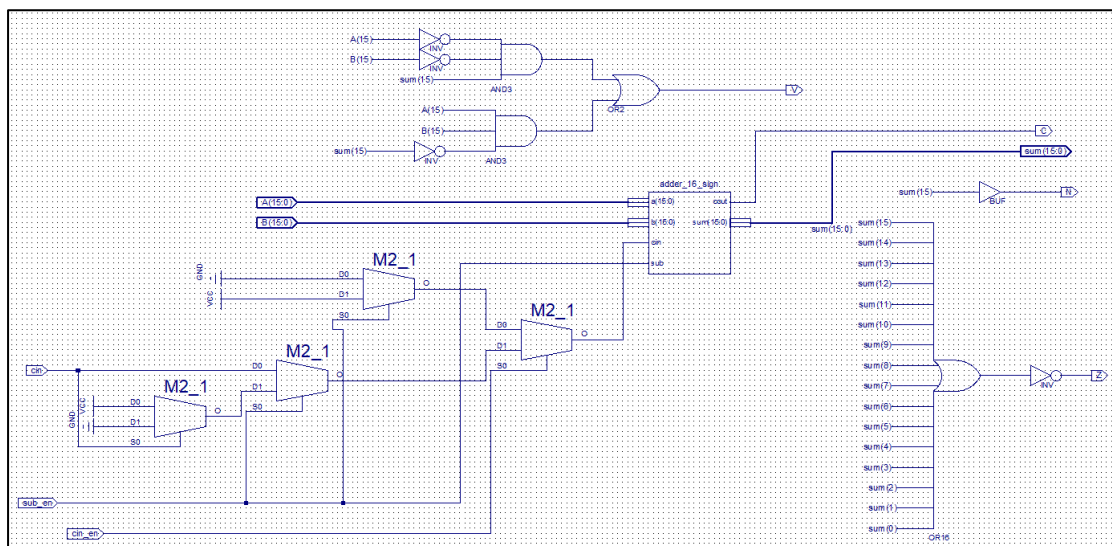


Adder_16_sign

 


✚ Adder_16

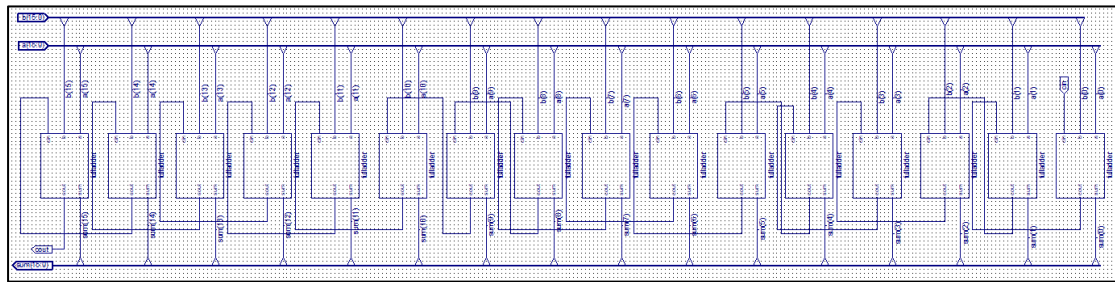


✚ fulladder

 


✚ Memory

 


✚ Instruction_Memory

 


Data_Memory

 


Memory_module_256_16

 

PC

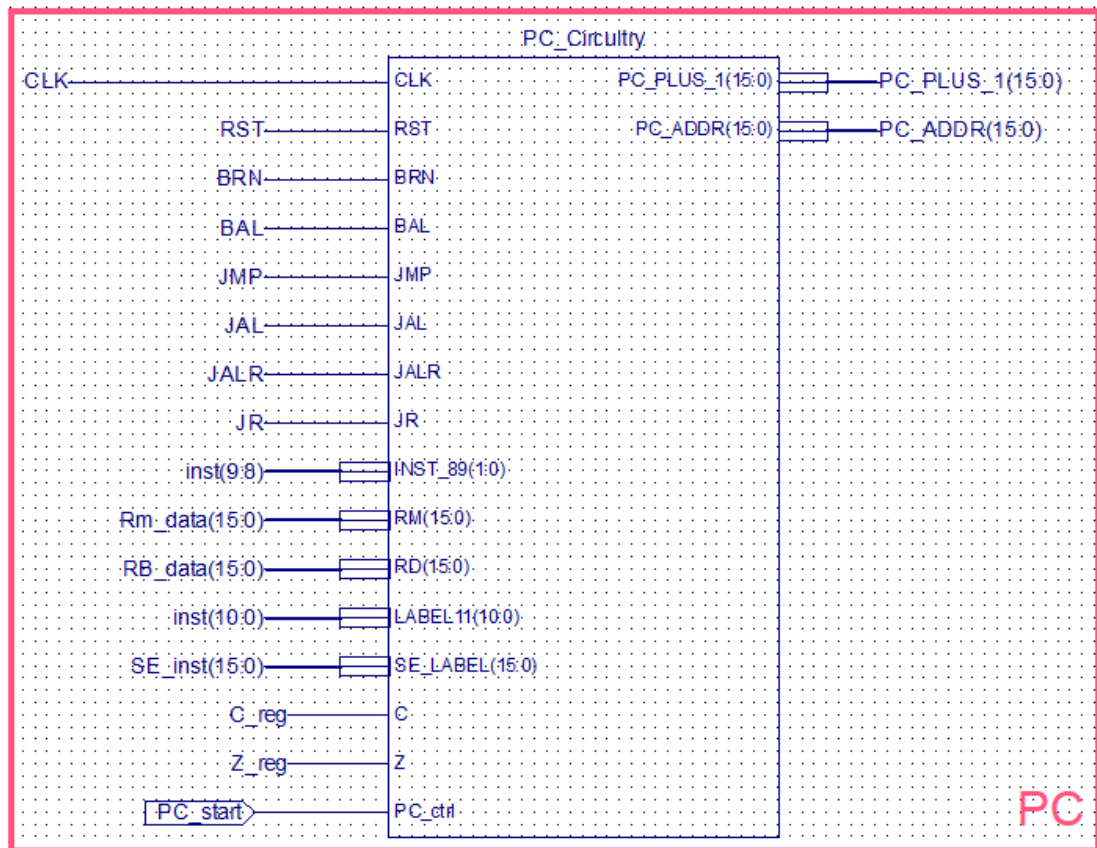

Controller

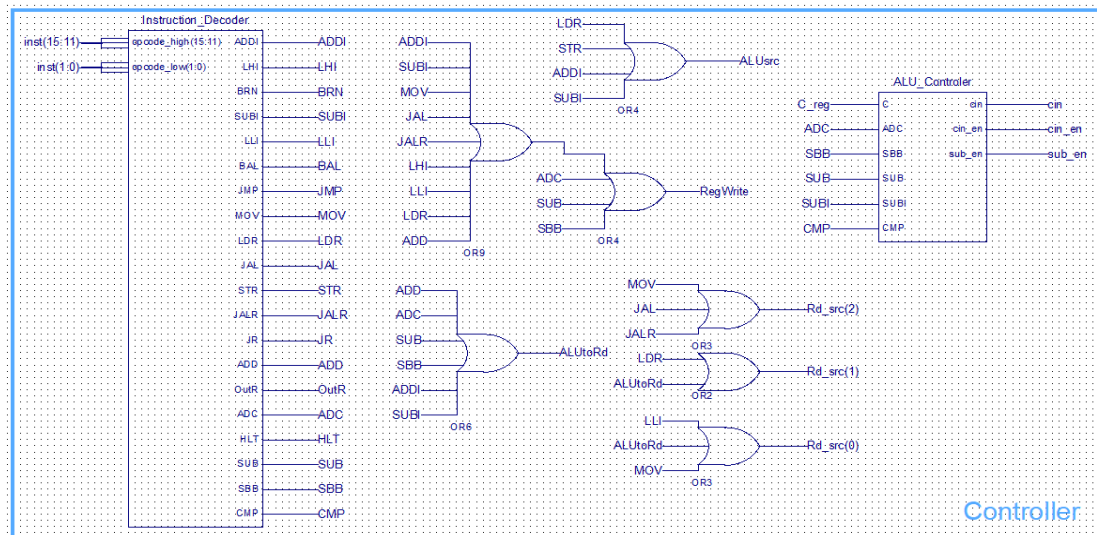


Verification

1. Find the minimum and maximum from two numbers in memory.


Assembly code

```
Main:
00  LLI R0, #25
02  LDR R1, R0, #0
04  LDR R2, R0, #1
06  OUTR R1
08  OUTR R2
0A  CMP R1, R2
0C  BCS R1_bigger
0E  MOV R1, R2
R1_bigger:
10  STR R1, R0, #2
12  OUTR R1
14  HLT
```

Behavioral

 

Post-Route

 

可以觀察到一開始記憶體裡面的值為 12H 和 18H，而在指令執行完後會找到最大值 18H 並輸出。

Testbench

```
`timescale 1ns / 1ps
module max_min_test;
    parameter clk_period = 40;
    parameter delay_factor = 2;
    // Inputs
    reg clk_in;
    reg rst_n;
    reg PC_start;
    reg ext_imem_w;
    reg [7:0] ext_i_addr;
    reg [15:0] ext_i_data;
    reg ext_i_addr_ctrl;
    reg ext_dmem_w;
    reg ext_d_addr_ctrl;
    reg ext_d_data_ctrl;
    reg [7:0] ext_d_addr;
    reg [15:0] ext_d_data;
    // Outputs
    wire [15:0] Out_R;
    wire done;
    // Instantiate the Unit Under Test (UUT)
    Single_Cycle_CPU uut (
        .clk_in(clk_in),
        .rst_n(rst_n),
        .Out_R(Out_R),
        .PC_start(PC_start),
        .done(done),
        .ext_imem_w(ext_imem_w),
        .ext_i_addr(ext_i_addr),
        .ext_i_data(ext_i_data),
        .ext_i_addr_ctrl(ext_i_addr_ctrl),
        .ext_dmem_w(ext_dmem_w),
        .ext_d_addr_ctrl(ext_d_addr_ctrl),
        .ext_d_data_ctrl(ext_d_data_ctrl),
        .ext_d_addr(ext_d_addr),
        .ext_d_data(ext_d_data)
    );
    initial begin
        // Initialize Inputs
        clk_in = 0;
        rst_n = 0;
        PC_start = 0;
        ext_imem_w = 0;
        ext_i_addr = 0;
        ext_i_data = 0;
        ext_i_addr_ctrl = 0;
        ext_dmem_w = 0;
        ext_d_addr_ctrl = 0;
        ext_d_data_ctrl = 0;
        ext_d_addr = 0;
        ext_d_data = 0;

        // Wait 100 ns for global reset to finish
        #100;

        // Add stimulus here
    end
    always begin
        #(clk_period/2) clk_in <= 1'b0;
        #(clk_period/2) clk_in <= 1'b1;
    end
end
```

```

initial begin
    rst_n <=1'b1;
    repeat(9)@(posedge clk_in)
        #(clk_period/delay_factor) rst_n <= 1'b0;
    rst_n <=1'b1;

    write_imem(8'h0, 16'b00010_000_00100101) ; //LLI R0,#25h
    write_imem(8'h1, 16'b00011_001_000_00000) ; //LDR R1, R0, #0
    write_imem(8'h2, 16'b00011_010_000_00001) ; //LDR R2, R0, #1
    write_imem(8'h3, 16'b11100_000_001_000_00) ; //OUTR R1 (20h)
    write_imem(8'h4, 16'b11100_000_010_000_00) ; //OUTR R2 (10h)
    write_imem(8'h5, 16'b00110_000_001_010_01) ; //CMP R1, R2
    write_imem(8'h6, 16'b1100_0010_00000010) ; //BCS R1_bigger
    write_imem(8'h7, 16'b01011_001_010_000_00) ; //MOV R1, R2.
    write_imem(8'h8, 16'b00101_001_000_00010) ; //STR R1, R0, #2
    write_imem(8'h9, 16'b11100_000_001_000_00) ; //OUTR R1 (20h)
    write_imem(8'hA, 16'b11100_0000_00000_01) ; //HLT
    write_dmem(8'h25, 16'h18 ) ; // data (25h, 18h)
    write_dmem(8'h26, 16'h12 ) ; // data (26h, 12h)
    // delay one clock to ensure the proper write to memory
    @(posedge clk_in) #(clk_period/delay_factor) begin
        ext_imem_w = 1'b0;
        ext_dmem_w = 1'b0;
        ext_i_addr_ctrl = 1'b0;
        ext_d_addr_ctrl = 1'b0;
        ext_d_data_ctrl = 1'b0;
    end
    // start the cpu to execute the program in memory
    @(posedge clk_in) #(clk_period/delay_factor) PC_start=1'b1;
    wait(done) ;
end
task write_imem;
    input [7:0] addr;
    input [15:0] data;
    begin
        @(posedge clk_in) #(clk_period/delay_factor) begin
            ext_imem_w = 1'b1;
            ext_i_addr_ctrl = 1'b1;
            ext_i_addr = addr;
            ext_i_data = data;
        end
    end
endtask
task write_dmem;
    input [7:0] addr;
    input [15:0] data;
    begin
        @(posedge clk_in) #(clk_period/delay_factor) begin
            ext_dmem_w = 1'b1;
            ext_d_addr_ctrl = 1'b1;
            ext_d_addr = addr;
            ext_d_data_ctrl = 1'b1;
            ext_d_data = data;
        end
    end
end
endtask

initial #10000 $finish ;
initial
    $monitor($realtime,"ns %h %h %h %h %h %h %h %h %h %h \n",
        clk_in , rst_n, ext_imem_w, ext_dmem_w, ext_i_addr_ctrl, ext_i_addr, ext_i_data, ext_d_
endmodule

```

2. Add two numbers in memory and store the result in another memory location.


Assembly code

```


Main:
00  LLI R0, #25
02  LDR R1, R0, #0
04  LDR R2, R0, #1
06  OUTR R1
08  OUTR R2
0A  ADD R3, R1, R2
0C  STR R3, R0, #2
0E  OUTR R3
10  HLT

```

Behavioral

 

Post-Route

 

把 47H 存在記憶體位址 0025H，0089H 存在記憶體位址 0026H，將兩數相加得到結果 00D0H，相減得到結果 FFBEH。



Testbench

```
module CPU_testbench;
    parameter clk_period = 40;
    parameter delay_factor = 2;
    // Inputs
    reg clk_in;
    reg rst_n;
    reg PC_start;
    reg ext_imem_w;
    reg [7:0] ext_i_addr;
    reg [15:0] ext_i_data;
    reg ext_i_addr_ctrl;
    reg ext_dmem_w;
    reg ext_d_addr_ctrl;
    reg ext_d_data_ctrl;
    reg [7:0] ext_d_addr;
    reg [15:0] ext_d_data;
    // Outputs
    wire [15:0] Out_R;
    wire done;
    // Instantiate the Unit Under Test (UUT)
    Single_Cycle_CPU uut (
        .clk_in(clk_in),
        .rst_n(rst_n),
        .Out_R(Out_R),
        .PC_start(PC_start),
        .done(done),
        .ext_imem_w(ext_imem_w),
        .ext_i_addr(ext_i_addr),
        .ext_i_data(ext_i_data),
        .ext_i_addr_ctrl(ext_i_addr_ctrl),
        .ext_dmem_w(ext_dmem_w),
        .ext_d_addr_ctrl(ext_d_addr_ctrl),
        .ext_d_data_ctrl(ext_d_data_ctrl),
        .ext_d_addr(ext_d_addr),
        .ext_d_data(ext_d_data)
    );
    initial begin
        // Initialize Inputs
        clk_in = 0;
        rst_n = 0;
        PC_start = 0;
        ext_imem_w = 0;
        ext_i_addr = 0;
        ext_i_data = 0;
        ext_i_addr_ctrl = 0;
        ext_dmem_w = 0;
        ext_d_addr_ctrl = 0;
        ext_d_data_ctrl = 0;
        ext_d_addr = 0;
        ext_d_data = 0;
        // Wait 100 ns for global reset to finish
        #100;
        // Add stimulus here
    end
    always begin
        #(clk_period/2) clk_in <= 1'b0;
        #(clk_period/2) clk_in <= 1'b1;
    end
end
```

```

initial begin
    rst_n <= 1'b1;
    repeat(9)@(posedge clk_in)
    # (clk_period/delay_factor) rst_n <= 1'b0;
    rst_n <= 1'b1;
    write_imem(8'h00, 16'b0001_0000_0010_0101 ) ; // LLI R0,#25
    write_imem(8'h01, 16'b0000_1000_0000_0000 ) ; // LHI R0,#00
    write_imem(8'h02, 16'b1110_0000_0000_0000 ) ; // OUT R0 (0025H)
    write_imem(8'h03, 16'b0001_1001_0000_0000 ) ; // LDR R1,R0,#0
    write_imem(8'h04, 16'b0001_1010_0000_0010 ) ; // LDR R2,R0,#2
    write_imem(8'h05, 16'b1110_0000_0010_0000 ) ; // OUT R1 (47H)
    write_imem(8'h06, 16'b1110_0000_0100_0000 ) ; // OUT R2 (89H)
    write_imem(8'h07, 16'b0000_0011_0010_1000 ) ; // ADD R3,R1,R2
    write_imem(8'h8, 16'b1110_0000_0110_0000 ) ; // OUT R3 (D0H)
    write_imem(8'h9, 16'b0000_0011_0010_1010 ) ; // SUB R3,R1,R2
    write_imem(8'hA, 16'b1110_0000_0110_0000 ) ; // OUT R3 (FFBEH)
    write_imem(8'hB, 16'b1110_0000_0000_0001 ) ; // HLT
    write_dmem(8'h25, 16'h47 ) ; // data (25h, 47h)
    write_dmem(8'h27, 16'h89 ) ; // data (27h, 89h)
    // delay one clock to ensure the proper write to memory
    @(posedge clk_in) # (clk_period/delay_factor) begin
        ext_imem_w = 1'b0;
        ext_dmem_w = 1'b0;
        ext_i_addr_ctrl = 1'b0;
        ext_d_addr_ctrl = 1'b0;
        ext_d_data_ctrl = 1'b0;
    end
    // start the cpu to execute the program in memory
    @(posedge clk_in) # (clk_period/delay_factor) PC_start=1'b1;
    wait(done) ;
end
task write_imem;
    input [7:0] addr;
    input [15:0] data;
    begin
        @(posedge clk_in) # (clk_period/delay_factor) begin
            ext_imem_w = 1'b1;
            ext_i_addr_ctrl = 1'b1;
            ext_i_addr = addr;
            ext_i_data = data;
        end
    end
endtask
task write_dmem;
    input [7:0] addr;
    input [15:0] data;
    begin
        @(posedge clk_in) # (clk_period/delay_factor) begin
            ext_dmem_w = 1'b1;
            ext_d_addr_ctrl = 1'b1;
            ext_d_addr = addr;
            ext_d_data_ctrl = 1'b1;
            ext_d_data = data;
        end
    end
endtask
initial #10000 $finish ;
initial
    $monitor($realtime,"ns %h %h %h %h %h %h %h %h %h \n",
        clk_in , rst_n, ext_imem_w, ext_dmem_w, ext_i_addr_ctrl, ext_i_addr,ext_i_data,
        ext_d_addr_ctrl, ext_d_addr, ext_d_data_ctrl, ext_d_data, Out_R, done);
endmodule

```

3. Add ten numbers in consecutive memory locations.


Assembly code

```


Main:
00    LLI R0, #25
02    LLI R3, #10
04    LLI R4, #1
06    LLI R2, #0
Loop:
08    LDR R1, R0, #0
0A    OUTR R1
0C    ADD R2, R2, R1
0E    ADDI R0, R0, 1

10    SUBI R3, R3, 1
12    CMP R3, R4
14    BCS Loop
16    STR R2, R0, #5
18    OUTR R2
1A    HLT
  
```

Behavioral

 

Post-Route

 

存在記憶體的值為 1~10，可以看到結果會將每次運算的值輸出出來，也就是會計算 $(1+2+3+\dots+9+10)=55$ ，並且得到 55 的正確答案。

Testbench

```
module ten_acc;
    parameter clk_period = 40;
    parameter delay_factor = 2;
    // Inputs
    reg clk_in;
    reg rst_n;
    reg PC_start;
    reg ext_imem_w;
    reg [7:0] ext_i_addr;
    reg [15:0] ext_i_data;
    reg ext_i_addr_ctrl;
    reg ext_dmem_w;
    reg ext_d_addr_ctrl;
    reg ext_d_data_ctrl;
    reg [7:0] ext_d_addr;
    reg [15:0] ext_d_data;
    // Outputs
    wire [15:0] Out_R;
    wire done;
    // Instantiate the Unit Under Test (UUT)
    Single_Cycle_CPU uut (
        .clk_in(clk_in),
        .rst_n(rst_n),
        .Out_R(Out_R),
        .PC_start(PC_start),
        .done(done),
        .ext_imem_w(ext_imem_w),
        .ext_i_addr(ext_i_addr),
        .ext_i_data(ext_i_data),
        .ext_i_addr_ctrl(ext_i_addr_ctrl),
        .ext_dmem_w(ext_dmem_w),
        .ext_d_addr_ctrl(ext_d_addr_ctrl),
        .ext_d_data_ctrl(ext_d_data_ctrl),
        .ext_d_addr(ext_d_addr),
        .ext_d_data(ext_d_data)
    );
    initial begin
        // Initialize Inputs
        clk_in = 0;
        rst_n = 0;
        PC_start = 0;
        ext_imem_w = 0;
        ext_i_addr = 0;
        ext_i_data = 0;
        ext_i_addr_ctrl = 0;
        ext_dmem_w = 0;
        ext_d_addr_ctrl = 0;
        ext_d_data_ctrl = 0;
        ext_d_addr = 0;
        ext_d_data = 0;
        // Wait 100 ns for global reset to finish
        #100;
        // Add stimulus here
    end
    always begin
        #(clk_period/2) clk_in <= 1'b0;
        #(clk_period/2) clk_in <= 1'b1;
    end
end
```

```

initial begin
    rst_n <= 1'b1;
    repeat(9)@(posedge clk_in)
    #(clk_period/delay_factor) rst_n <= 1'b0;
    rst_n <= 1'b1;
    write_imem(8'h0, 16'b00010_000_00100101) ; //LLI R0, #25h
    write_imem(8'h1, 16'b00010_011_00001010) ; //LLI R3, #10
    write_imem(8'h2, 16'b00010_100_00000001) ; //LLI R4, #1
    write_imem(8'h3, 16'b00010_010_00000000) ; //LLI R2, #0
    write_imem(8'h4, 16'b00011_001_000_00000) ; //LDR R1, R0, #0
    write_imem(8'h5, 16'b11100_000_001_000_00) ; //OUTR R1 (1,2,3,4,5,6,7,8,9)
    write_imem(8'h6, 16'b00000_010_010_001_00) ; //ADD R2, R2, R1
    write_imem(8'h7, 16'b00111_000_000_00001) ; //ADDI R0, R0, 1
    write_imem(8'h8, 16'b01000_011_011_00001) ; //SUBI R3, R3, 1
    //write_imem(8'h9, 16'b11100_000_011_000_00) ; //OUTR R3 ////
    write_imem(8'h9, 16'b00110_000_011_100_01) ; //CMP R3, R4
    write_imem(8'hA, 16'b1100_0010_11111010) ; //BCS Loop ////
    write_imem(8'hB, 16'b00101_010_000_00101) ; //STR R2, R0, #5
    write_imem(8'hC, 16'b11100_000_010_000_00) ; //OUTR R2 (45)
    write_imem(8'hD, 16'b11100_0000_00000_01) ; //HLT
    write_dmem(8'h25, 16'h1 ) ; // data (25h, 1h)
    write_dmem(8'h26, 16'h2 ) ; // data (26h, 2h)
    write_dmem(8'h27, 16'h3 ) ; // data (27h, 3h)
    write_dmem(8'h28, 16'h4 ) ; // data (28h, 4h)
    write_dmem(8'h29, 16'h5 ) ; // data (29h, 5h)
    write_dmem(8'h2A, 16'h6 ) ; // data (2Ah, 6h)
    write_dmem(8'h2B, 16'h7 ) ; // data (2Bh, 7h)
    write_dmem(8'h2C, 16'h8 ) ; // data (2Ch, 8h)
    write_dmem(8'h2D, 16'h9 ) ; // data (2Dh, 9h)
    write_dmem(8'h2E, 16'hA ) ; // data (2Eh, Ah)
    // delay one clock to ensure the proper write to memory
    @(posedge clk_in) #(clk_period/delay_factor) begin
        ext_imem_w = 1'b0;
        ext_dmem_w = 1'b0;

        ext_i_addr_ctrl = 1'b0;
        ext_d_addr_ctrl = 1'b0;
        ext_d_data_ctrl = 1'b0;
    end
    // start the cpu to execute the program in memory
    @(posedge clk_in) #(clk_period/delay_factor) PC_start=1'b1;
    wait(done) ;
end
task write_imem;
    input [7:0] addr;
    input [15:0] data;
    begin
        @(posedge clk_in) #(clk_period/delay_factor) begin
            ext_imem_w = 1'b1;
            ext_i_addr_ctrl = 1'b1;
            ext_i_addr = addr;
            ext_i_data = data;
        end
    end
endtask
task write_dmem;
    input [7:0] addr;
    input [15:0] data;
    begin
        @(posedge clk_in) #(clk_period/delay_factor) begin
            ext_dmem_w = 1'b1;
            ext_d_addr_ctrl = 1'b1;
            ext_d_addr = addr;
            ext_d_data_ctrl = 1'b1;
            ext_d_data = data;
        end
    end
endtask
initial #10000 $finish ;
initial
    $monitor($realtime, "ns %h %h %h %h %h %h %h %h %h \n",
        clk_in , rst_n, ext_imem_w, ext_dmem_w, ext_i_addr_ctrl, ext_i_addr, ext_i_data,
        ext_d_addr_ctrl, ext_d_addr, ext_d_data_ctrl, ext_d_data, Out_R, done);
endmodule

```

- Mov a memory block of N words from one place to another.


Assembly code

```


Main:
00    LLI R0, #25h
02    LLI R2, #10
04    LLI R3, #1
06    LLI R4, #39
Loop:
08    LDR R1, R0, #0
0A    OUTR R1
0C    STR R1, R0, #30
0E    ADDI R0, R0, #1
10    SUBI R2, R2, #1
12    CMP R2, R3
14    BCS Loop
16    LLI R2, #10
Loop_check:
18    LDR R1, R4, #0
1A    OUTR R1
1C    ADDI R4, R4, #1
1E    SUBI R2, R2, #1
20    CMP R2, R3
22    BCS Loop_check
24    HLT

```

Behavioral

 

Post-Route

 

可以看到最後的輸出是 8...9...10，因為我們是將 memory 裡面的 1~10，搬到另一個記憶體位址，我們再搬完後去查看記憶體的位址裡面是否為 1~10，可以發現 move 成功。

Testbench

```
module mov_10;
    parameter clk_period = 40;
    parameter delay_factor = 2;
    // Inputs
    reg clk_in;
    reg PC_start;
    reg rst_n;
    reg ext_imem_w;
    reg ext_d_data_ctrl;
    reg [7:0] ext_i_addr;
    reg [15:0] ext_i_data;
    reg ext_i_addr_ctrl;
    reg ext_dmem_w;
    reg ext_d_addr_ctrl;
    reg [7:0] ext_d_addr;
    reg [15:0] ext_d_data;
    // Outputs
    wire [15:0] Out_R;
    wire done;
    // Instantiate the Unit Under Test (UUT)
    Single_Cycle_CPU uut (
        .clk_in(clk_in),
        .rst_n(rst_n),
        .Out_R(Out_R),
        .done(done),
        .ext_imem_w(ext_imem_w),
        .PC_start(PC_start),
        .ext_i_addr(ext_i_addr),
        .ext_i_data(ext_i_data),
        .ext_d_data_ctrl(ext_d_data_ctrl),
        .ext_i_addr_ctrl(ext_i_addr_ctrl),
        .ext_d_addr_ctrl(ext_d_addr_ctrl),
        .ext_dmem_w(ext_dmem_w),
        .ext_d_addr(ext_d_addr),
        .ext_d_data(ext_d_data)
    );
    initial begin
        // Initialize Inputs
        clk_in = 0;
        rst_n = 1;
        ext_imem_w = 0;
        ext_i_addr = 0;
        ext_i_data = 0;
        ext_dmem_w = 0;
        ext_d_addr = 0;
        ext_d_data = 0;

        // Wait 100 ns for global reset to finish
        #100;
        // Add stimulus here
    end
    // generate the clock signal
    always begin
        #(clk_period/2) clk_in <= 1'b0;
        #(clk_period/2) clk_in <= 1'b1;
    end
end
```

```

initial begin
rst_n <=1'b0;
repeat(9)@(posedge clk_in)
#(clk_period/delay_factor) rst_n <= 1'b0;PC_start <= 1'b0;
#(clk_period/delay_factor) rst_n <=1'b1;
write_imem(8'h0, 16'b00010_000_00100101) ; //LLI R0,#25h
write_imem(8'h1, 16'b00010_010_00001010) ; //LLI R2, #10
write_imem(8'h2, 16'b00010_011_00000001) ; //LLI R3, #1
write_imem(8'h3, 16'b00010_100_00111001) ; //LLI R4, #39h
write_imem(8'h4, 16'b00011_001_000_00000) ; //LDR R1, R0, #0
write_imem(8'h5, 16'b11100_000_001_000_00) ; //OUTR R1 (1,2,3,4,5,6,7,8,9,10)
write_imem(8'h6, 16'b00101_001_000_10100) ; //STR R1, R0, #20
write_imem(8'h7, 16'b00111_000_000_00001) ; //ADDI R0, R0, 1
write_imem(8'h8, 16'b01000_010_010_00001) ; //SUBI R2, R2, 1
write_imem(8'h9, 16'b00110_000_010_011_01) ; //CMP R2, R3
write_imem(8'hA, 16'b1100_0010_11111010) ; //BCS Loop
write_imem(8'hB, 16'b00010_010_00001010) ; //LLI R2, #10
write_imem(8'hC, 16'b00011_001_100_00000) ; //LDR R1, R4, #0
write_imem(8'hD, 16'b11100_000_001_000_00) ; //OUTR R1 (1,2,3,4,5,6,7,8,9,10)
write_imem(8'hE, 16'b00111_100_100_00001) ; //ADDI R4, R4, #1
write_imem(8'hF, 16'b01000_010_010_00001) ; //SUBI R2, R2, #1
write_imem(8'h10, 16'b00110_000_010_011_01) ; //CMP R2, R3
write_imem(8'h11, 16'b1100_0010_11111011) ; //BCS Loop_check
write_imem(8'h12, 16'b11100_0000_00000_01) ; //HLT
write_dmem(8'h25, 16'h1 ) ; // data (25h, 1h)
write_dmem(8'h26, 16'h2 ) ; // data (26h, 2h)
write_dmem(8'h27, 16'h3 ) ; // data (27h, 3h)
write_dmem(8'h28, 16'h4 ) ; // data (28h, 4h)
write_dmem(8'h29, 16'h5 ) ; // data (29h, 5h)
write_dmem(8'h2A, 16'h6 ) ; // data (2Ah, 6h)
write_dmem(8'h2B, 16'h7 ) ; // data (2Bh, 7h)
write_dmem(8'h2C, 16'h8 ) ; // data (2Ch, 8h)
write_dmem(8'h2D, 16'h9 ) ; // data (2Dh, 9h)
write_dmem(8'h2E, 16'hA ) ; // data (2Eh, Ah)


// delay one clock to ensure the proper write to memory
@(posedge clk_in) #(clk_period/delay_factor) begin
ext_imem_w = 1'b0;
ext_dmem_w = 1'b0;
ext_i_addr_ctrl = 1'b0;
ext_d_addr_ctrl = 1'b0;
ext_d_data_ctrl = 1'b0;
end
// start the cpu to execute the program in memory
@(posedge clk_in) #(clk_period/delay_factor) PC_start=1'b1;
wait(done) ;
end
task write_imem;
input [7:0] addr;
input [15:0] data;
begin
@(posedge clk_in) #(clk_period/delay_factor) begin
ext_imem_w = 1'b1;
ext_i_addr_ctrl = 1'b1;
ext_i_addr = addr;
ext_i_data = data;
end
end
endtask
task write_dmem;
input [7:0] addr;
input [15:0] data;
begin
@(posedge clk_in) #(clk_period/delay_factor) begin
ext_dmem_w = 1'b1;
ext_d_addr_ctrl = 1'b1;
ext_d_addr = addr;
ext_d_data_ctrl = 1'b1;
ext_d_data = data;
end
end
endtask
initial #10000 $finish ;
initial
$monitor($realtime,"ns %h %h %h %h %h %h %h %h %h \n",
clk_in , rst_n, ext_imem_w, ext_dmem_w, ext_i_addr_ctrl, ext_i_addr, ext_i_data,
ext_d_addr_ctrl, ext_d_addr, ext_d_data_ctrl, ext_d_data, Out_R, done);
endmodule

```


Hardware

Device Utilization Summary:				
Slice Logic Utilization:				
Number of Slice Registers:	148 out of	93,120	1%	
Number used as Flip Flops:	146			
Number used as Latches:	0			
Number used as Latch-thrus:	0			
Number used as AND/OR logics:	2			
Number of Slice LUTs:	889 out of	46,560	1%	
Number used as logic:	754 out of	46,560	1%	
Number using O6 output only:	661			
Number using O5 output only:	29			
Number using O5 and O6:	64			
Number used as ROM:	0			
Number used as Memory:	132 out of	16,720	1%	
Number used as Dual Port RAM:	0			
Number used as Single Port RAM:	132			
Number using O6 output only:	132			
Number using O5 output only:	0			
Number using O5 and O6:	0			
Number used as Shift Register:	0			
Number used exclusively as route-thrus:	3			
Number with same-slice register load:	0			
Number with same-slice carry load:	3			
Number with other load:	0			
Slice Logic Distribution:				
Number of occupied Slices:	343 out of	11,640	2%	
Number of LUT Flip Flop pairs used:	889			
Number with an unused Flip Flop:	741 out of	889	83%	
Number with an unused LUT:	0 out of	889	0%	
Number of fully used LUT-FF pairs:	148 out of	889	16%	
Number of slice register sites lost to control set restrictions:	0 out of	93,120	0%	
<p>A LUT Flip Flop pair for this architecture represents one LUT paired with one Flip Flop within a slice. A control set is a unique combination of clock, reset, set, and enable signals for a registered element.</p> <p>The Slice Logic Distribution report is not meaningful if the design is over-mapped for a non-slice resource or if Placement fails.</p> <p>OVERMAPPING of BRAM resources should be ignored if the design is over-mapped for a non-BRAM resource or if placement fails.</p>				
IO Utilization:				
Number of bonded IOBs:	73 out of	240	30%	
Specific Feature Utilization:				
Number of RAMB36E1/FIFO36E1s:	0 out of	156	0%	
Number of RAMB18E1/FIFO18E1s:	0 out of	312	0%	
Number of BUFG/BUFGCTRLs:	1 out of	32	3%	
Number used as BUFGs:	1			
Number used as BUFGCTRLs:	0			
Number of ILOGIC1/ISERDESE1s:	0 out of	360	0%	
Number of OLOGIC1/OSERDESE1s:	0 out of	360	0%	
Number of BSCANs:	0 out of	4	0%	
Number of BUFHCEs:	0 out of	72	0%	
Number of BUFIODQs:	0 out of	36	0%	
Number of BUFRs:	0 out of	18	0%	
Number of CAPTUREs:	0 out of	1	0%	
Number of DSP48E1s:	0 out of	288	0%	
Number of EFUSE_USRs:	0 out of	1	0%	
Number of FRAME_ECCs:	0 out of	1	0%	
Number of GTXE1s:	0 out of	8	0%	
Number of IBUFDS_GTXE1s:	0 out of	6	0%	
Number of ICAPs:	0 out of	2	0%	
Number of IDELAYCTRLs:	0 out of	9	0%	
Number of IODELAYE1s:	0 out of	360	0%	
Number of MMCM_ADVs:	0 out of	6	0%	
Number of PCIE_2_0s:	0 out of	1	0%	
Number of STARTUPs:	1 out of	1	100%	
Number of SYMONs:	0 out of	1	0%	
Number of TEMAC_SINGLES:	0 out of	4	0%	

FPGA VIEW

 

RTL VIEW:

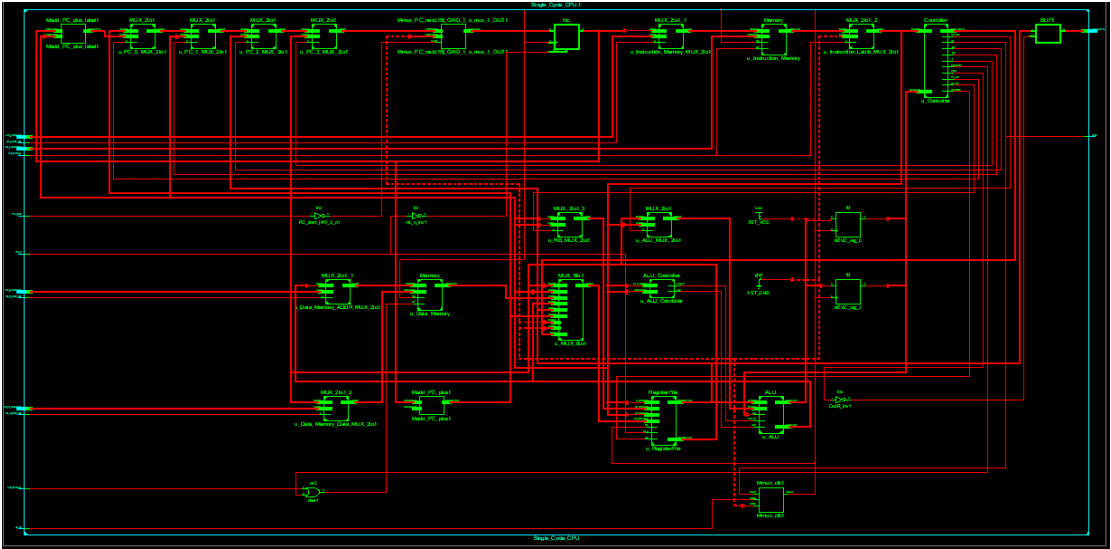

Discussion

這次的作業就是根據期中的 Schematic 電路，使用 verilog 硬體描述語言來實現，而由於期中的使用已經做過 Schematic 的版本，因此實作起來並沒有想像中困難，反而覺得 Schematic 電路在設計上想得比較多，這可能就是銘波老師上課常說的 Hardware mind 也就是因為要有硬體思維，寫 verilog 時心中必須有那個電路的架構，而不是使用平常寫 c 語言等等軟體思維再進行，用軟體思維在實作的話除了可能會寫出無法合成的電路外，時常自己可能也不知道合成出來的電路是什麼。

因此很感謝老師這一學期的教導，除了讓我學會很多作為數位 IC 工程師該有的知識與技能外，也培養了我解決問題的能力與該具備的硬體思維，老師上課所使用的課本也寫了許多很重要的概念，可能到未來面試或工作都還會使用到，希望未來能夠繼續在此精進自己。